

SAMPLE
PSPICE
REPORT

PSPICE Assignment #1

John Doe
EGR 299
Electrical Circuits 1
Due date: 9-9-99


Problem Description:

1. Bridge Circuit with Known Resistances

- Analyze the circuit below when $R_6 = 2 \text{ k}\Omega$ by hand in order to determine the values of I_4 and V_6 .
- Analyze the circuit below using PSpice when $R_6 = 2 \text{ k}\Omega$. Use a current printer and a voltage printer to print the values of I_4 and V_6 .
- Compare the results of step A and step B in a table.

Preliminary Analysis:

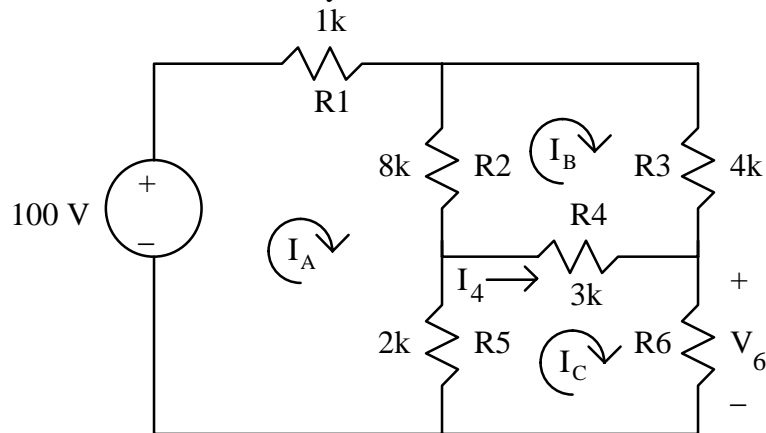Analyze the circuit below when $R_6 = 2 \text{ k}\Omega$ by hand in order to determine the values of I_4 and V_6 .



Mesh Analysis is used to first solve for I_A , I_B , and I_C :

$$\text{KVL, mesh A: } -100 + 1I_A + 8(I_A - I_B) + 2(I_A - I_C) = 0$$

$$\text{KVL, mesh B: } 4I_B + 3(I_B - I_C) + 8(I_B - I_A) = 0$$

$$\text{KVL, mesh C: } 2I_C + 2(I_C - I_A) + 3(I_C - I_B) = 0$$

$$\begin{bmatrix} 11 & -8 & -2 \\ -8 & 15 & -3 \\ -2 & -3 & 7 \end{bmatrix} \cdot \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \\ 0 \end{bmatrix} \quad \text{so} \quad \begin{aligned} I_A &= 21.24 \text{ mA} \\ I_B &= 13.72 \text{ mA} \\ I_C &= 11.95 \text{ mA} \end{aligned}$$

$$I_4 = I_C - I_B = 11.95 - 13.72$$

$$\boxed{I_4 = -1.77 \text{ mA}}$$


$$V_6 = R_6 \cdot I_C = (2 \text{ k}\Omega)(11.95 \text{ mA})$$

$$\boxed{V_6 = 23.9 \text{ V}}$$

**BOX YOUR
FINAL
ANSWERS**

Assignment #1 - Problem 1

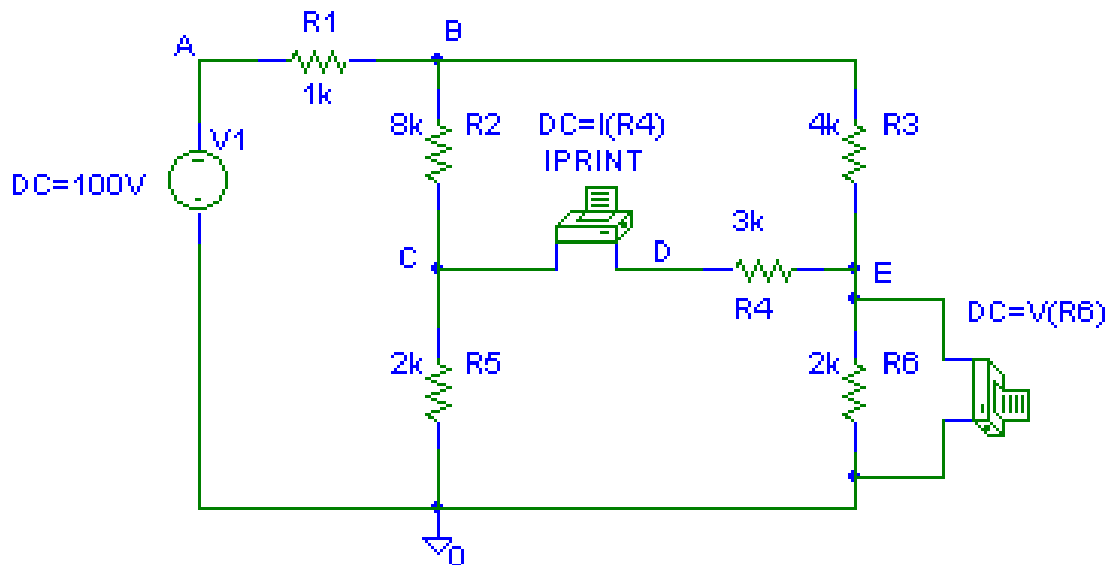Purpose: Determine the current through R4 and the voltage across R6 in case where $R6 = 2000$ ohms.



Hints for good schematics:

- Include name, course, Assignment Number
- Label all nodes
- Include a Purpose statement
- Display all attributes that are changed, such as source voltages, variables to be printed, ranges over which a quantity is varied, etc.
- Identify any variables (such as voltages or currents referred to in the problem)
- Use component names identical to the ones used in the hand analysis
- Other useful comments

**** 09/27/99 12:45:18 ***** NT Evaluation PSpice (July 1997) *****

* H:\EGR271\PSPICE\PS_SAMP1.sch

**** CIRCUIT DESCRIPTION

* Schematics Version 8.0 - July 1997

* Mon Sep 27 12:45:16 1999

** Analysis setup **

.DC LIN V_V1 100 100 1

.OP

* From [SCHEMATICS NETLIST] section of msim.ini:

.lib nom.lib

.INC "PS_SAMP1.net"

**** INCLUDING PS_SAMP1.net ****

* Schematics Netlist *

R_R1 A B 1k

V_PRINT1 C D 0V

.PRINT DC I(V_PRINT1)

.PRINT DC V([E],[0])

V_V1 A 0 DC 100V

R_R2 B C 8k

R_R5 C 0 2k

R_R3 B E 4k

R_R6 E 0 2k

R_R4 E D 3k

.probe

.END

**Be sure to include
the NETLIST with
each circuit**

**** 09/27/99 12:45:18 ***** NT Evaluation PSpice (July 1997) *****

* H:\EGR271\PSPICE\PS_SAMP1.sch

**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C

V_V1 I(V_PRINT1)

1.000E+02 -1.770E-03 so I(R4) = -1.77 mA

*Be sure to highlight
and clearly define
appropriate outputs*

**** 09/27/99 12:45:18 ***** NT Evaluation PSpice (July 1997) *****

* H:\EGR271\PSPICE\PS_SAMP1.sch

**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C

V_V1 V(E,0)

1.000E+02 2.389E+01 so V(R6) = 23.89 V

**** 09/27/99 12:45:18 ***** NT Evaluation PSpice (July 1997) *****

* H:\EGR271\PSPICE\PS_SAMP1.sch

**** SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C

NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE

(A) 100.0000 (B) 78.7610 (C) 18.5840 (D) 18.5840 (E) 23.8940

VOLTAGE SOURCE CURRENTS

NAME CURRENT

V_PRINT1 -1.770E-03

V_V1 -2.124E-02

TOTAL POWER DISSIPATION 2.12E+00 WATTS

JOB CONCLUDED

TOTAL JOB TIME .21

Analysis/Discussion:

The results of the hand analysis and the PSPICE analysis for Problem 1 are shown in the table below. All results are in agreement.


Value	Hand Results	PSPICE Results
I(R4)	-1.77 mA	23.9 V
V(R6)	-1.77 mA	23.89 V

**Be sure
to compare hand
results and PSPICE
results (in a table)
whenever possible.**

Problem Description:

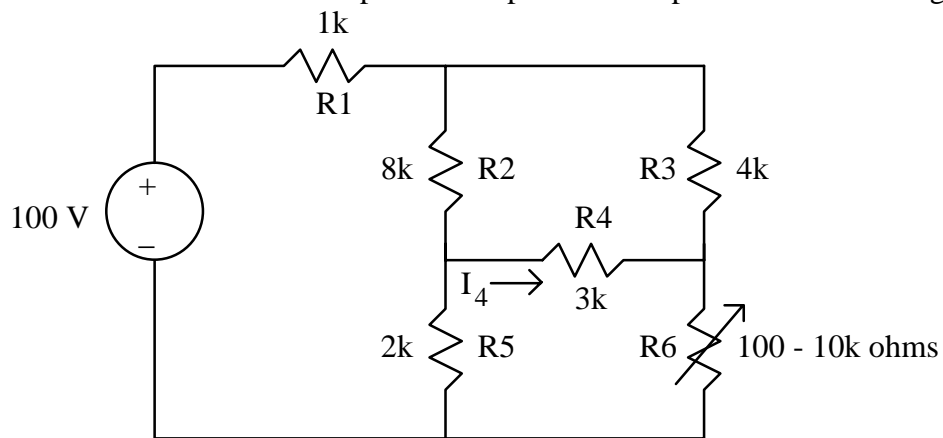2. Bridge Circuit with a Variable Resistor


- Analyze the circuit below where R_6 is varied from $100\ \Omega$ to $10\ \text{k}\Omega$ (use 25 points per decade).
- Use PROBE to graph I_4 versus R_6 . Place a cursor on the graph where $R_6 = 2\ \text{k}\Omega$ and mark the point.
- Place a cursor on the graph where $I_4 = 0$ and mark the point. This point shows the value of R_6 required to make $I_4 = 0$.
- Compare the value of I_4 revealed in step 2B with the value of I_4 determined in step 1B.
- The current I_4 should equal zero when the bridge circuit is “balanced”. Verify that the value of R_6 determined in step 2C corresponds to the point where the bridge is balanced.



Preliminary Analysis: None required

Assignment #1 - Problem 2

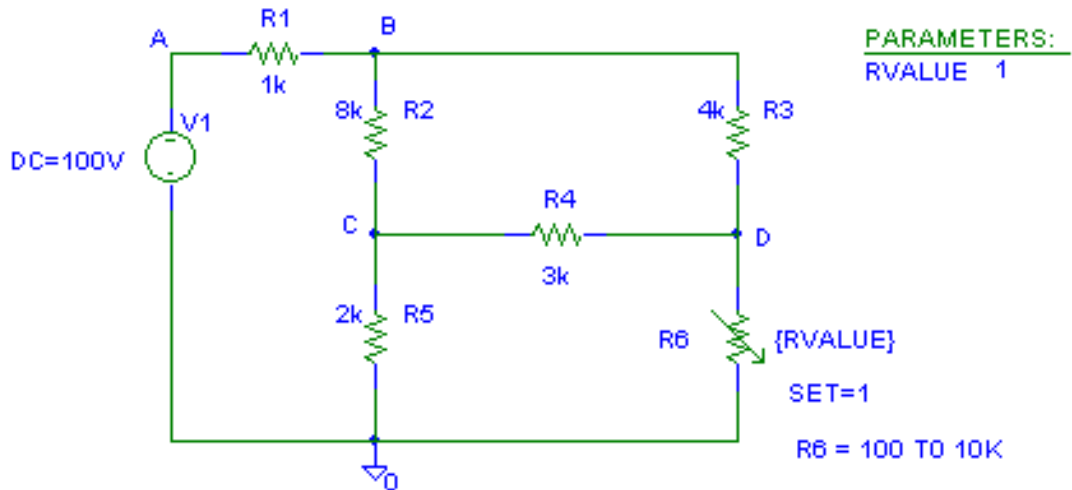Purpose: Vary resistor R6 from 100 ohms to 10,000 ohms and use PROBE to plot I(R4) versus R6.



* H:\EGR271\PS_PICE\PS_SAMP2.sch

**** CIRCUIT DESCRIPTION

* Schematics Version 8.0 - July 1997

* Mon Sep 27 13:23:30 1999

.PARAM RVALUE=1

** Analysis setup **

.DC LIN PARAM RVALUE 100 10K 25

.OP

* From [SCHEMATICS NETLIST] section of msim.ini:

.lib nom.lib

.INC "PS_SAMP2.net"

**** INCLUDING PS_SAMP2.net ****

* Schematics Netlist *

R_R1 A B 1k
V_V1 A 0 DC 100V
R_R2 B C 8k
R_R5 C 0 2k
R_R3 B D 4k
R_R4 C D 3k
R_R6 D 0 {{RVALUE}*1+.001}

.probe

.END

VOLTAGE SOURCE CURRENTS


NAME	CURRENT
V_V1	-2.640E-02

TOTAL POWER DISSIPATION 2.64E+00 WATTS

JOB CONCLUDED

TOTAL JOB TIME .69

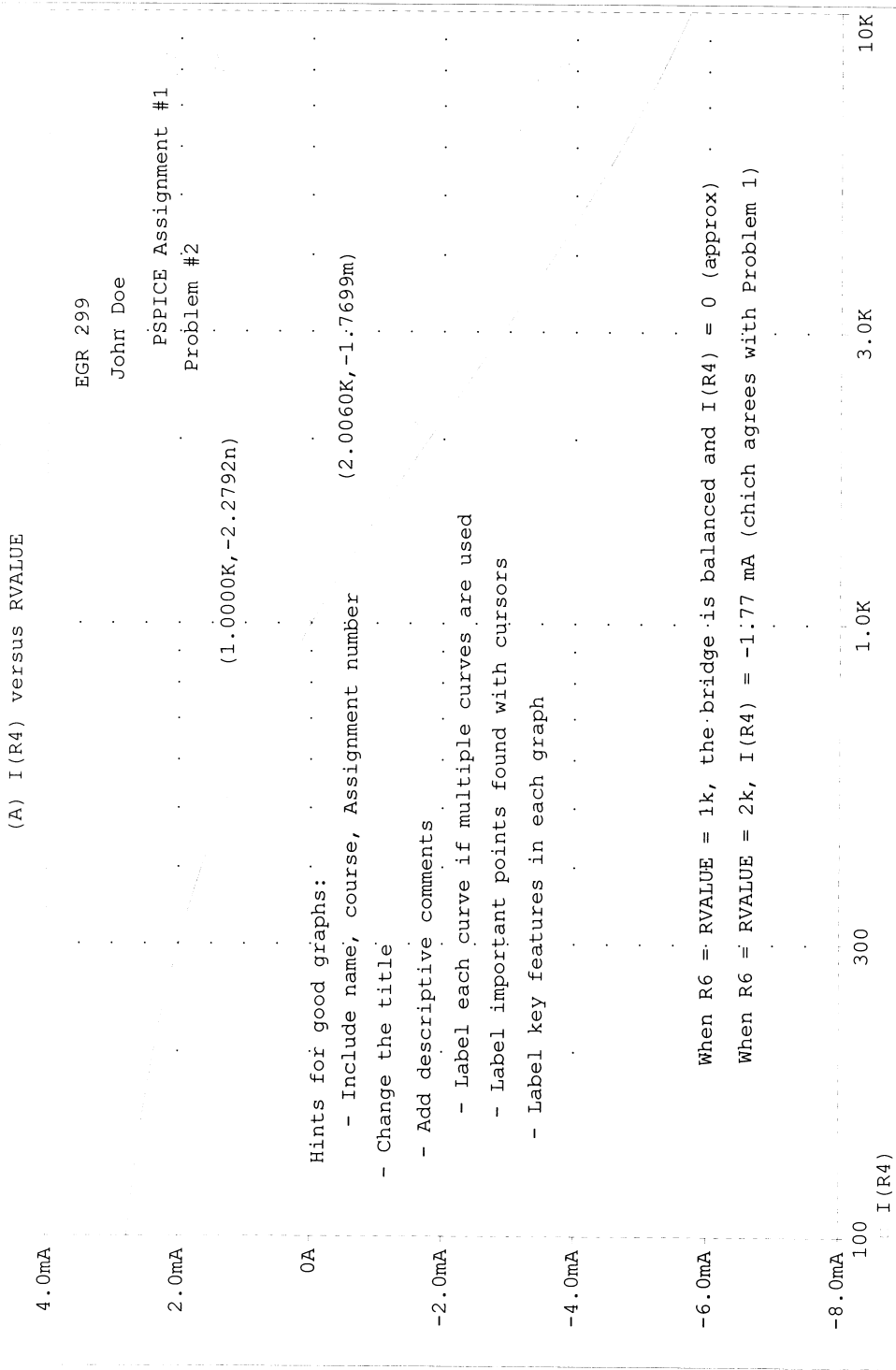Be sure to include the .OUT file (at least the parts containing the NETLIST and any required outputs).



Analysis/Discussion:

The graph of $I(R4)$ versus $R6$ generated using PROBE shows that $I(R4)$ varies over a wide range of positive and negative values as $R6$ is varied. Two points of special interest are marked on the graph:

- 1) A point was marked where $R6 = 2 \text{ k}\Omega$ (as close as possible). This corresponds to the circuit analyzed in Problem 1 where $R6$ was a fixed resistor with value $2 \text{ k}\Omega$. The result in both cases is the same: $I(R4) = -1.77 \text{ mA}$. This also agrees with the hand analysis, as seen in Problem 1.
- 2) A point was marked where $I(R4) = 0$ (as close as possible). It is a known fact that this current should be zero when the bridge is “balanced”, i.e., when $R2 \cdot R6 = R3 \cdot R5$. Since $R2$, $R3$, and $R5$ are fixed resistors, it is possible to solve for the value of $R6$ required for a balanced bridge, as shown below:

$$R6 = \frac{R3 \cdot R5}{R2} = \frac{4 \text{ k}\Omega \cdot 2 \text{ k}\Omega}{8 \text{ k}\Omega} = 1 \text{ k}\Omega$$

This result is verified by the graph where it is marked that $I(R4) = 0$ when $R6 = 1 \text{ k}\Omega$.

PSPICE Assignment #1

**Attached
Assignment
Sheet
(optional)**

1. Bridge Circuit with Known Resistances

- Analyze the circuit below when $R_6 = 2 \text{ k}\Omega$ by hand in order to determine the values of I_4 and V_6 .
- Analyze the circuit below using PSPICE when $R_6 = 2 \text{ k}\Omega$. Use a current printer and a voltage printer to print the values of I_4 and V_6 .
- Compare the results of step A and step B in a table.

2. Bridge Circuit with a Variable Resistor

- Analyze the circuit below where R_6 is varied from 100Ω to $10 \text{ k}\Omega$ (use 25 points per decade).
- Use PROBE to graph I_4 versus R_6 . Place a cursor on the graph where $R_6 = 2 \text{ k}\Omega$ and mark the point.
- Place a cursor on the graph where $I_4 = 0$ and mark the point. This point shows the value of R_6 required to make $I_4 = 0$.
- Compare the value of I_4 revealed in step 2B with the value of I_4 determined in step 1B.
- The current I_4 should equal zero when the bridge circuit is "balanced". Verify that the value of R_6 determined in step 2C corresponds to the point where the bridge is balanced.

