

EGR 260

Circuit Analysis

File: N260H11BS

## Solution to Homework Assignment #11

**Problem Assignment:** Ch 8 in Electric Circuits, 8<sup>th</sup> Edition by Nilsson

1) Chapter 8 problems: 3, 4, 6, 30, 35, 38, 40, 44, 51

P 8.3 [a]  $\alpha = 4000$ ;  $\omega_d = 3000$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2}$$

$$\therefore \omega_o^2 = \omega_d^2 + \alpha^2 = 9 \times 10^6 + 16 \times 10^6 = 25 \times 10^6$$

$$\frac{1}{LC} = 25 \times 10^6$$

$$L = \frac{1}{(25 \times 10^6)(50 \times 10^{-9})} = 0.8 \text{ H} = 800 \text{ mH}$$

$$[\text{b}] \alpha = \frac{1}{2RC}$$

$$\therefore R = \frac{1}{2\alpha C} = \frac{10^9}{(8000)(50)} = 2500 \Omega$$

$$[\text{c}] V_o = v(0) = 125 \text{ V}$$

$$[\text{d}] I_o = i_L(0) = -i_R(0) - i_C(0)$$

$$i_R(0) = \frac{V_o}{R} = \frac{125}{2.5} \times 10^{-3} = 50 \text{ mA}$$

$$i_C(0) = C \frac{dv}{dt}(0)$$

$$\frac{dv}{dt} = 125 \{ e^{-4000t} [-3000 \sin 3000t - 6000 \cos 3000t] -$$

$$4000 e^{-4000t} [\cos 3000t - 2 \sin 3000t]$$

$$\frac{dv}{dt}(0) = 125 \{ 1(-6000) - 4000 \} = -125 \times 10^4$$

$$C \frac{dv}{dt}(0) = -125 \times 10^4 (50 \times 10^{-9}) = -6250 \times 10^{-5} = -62.5 \text{ mA}$$

$$\therefore I_o = -50 + 62.5 = 12.5 \text{ mA}$$

$$[\text{e}] \frac{dv}{dt} = 125 e^{-4000t} [5000 \sin 3000t - 10,000 \cos 3000t]$$

$$= 625 \times 10^3 e^{-4000t} [\sin 3000t - 2 \cos 3000t]$$

$$C \frac{dv}{dt} = 31,250 \times 10^{-6} e^{-4000t} (\sin 3000t - 2 \cos 3000t)$$

$$i_C(t) = 31.25 e^{-4000t} (\sin 3000t - 2 \cos 3000t) \text{ mA}$$

$$i_R(t) = 50 e^{-4000t} (\cos 3000t - 2 \sin 3000t) \text{ mA}$$

$$i_L(t) = -i_R(t) - i_C(t)$$

$$= e^{-4000t} (12.5 \cos 3000t + 68.75 \sin 3000t) \text{ mA}, \quad t \geq 0$$

CHECK:

$$\frac{di_L}{dt} = \{-4000 e^{-4000t} [12.5 \cos 3000t + 68.75 \sin 3000t]$$

$$+ e^{-4000t} [-37.5 \times 10^3 \sin 3000t$$

$$+ 206.25 \times 10^3 \cos 3000t] \times 10^{-3}$$

$$= e^{-4000t} [156.25 \cos 3000t - 312.5 \sin 3000t]$$

$$L \frac{di_L}{dt} = e^{-4000t} [125 \cos 3000t - 250 \sin 3000t]$$

$$= 125 e^{-4000t} [\cos 3000t - 2 \sin 3000t] \text{ V}$$

$$\text{P 8.4 [a]} \quad \left(\frac{1}{2RC}\right)^2 = \frac{1}{LC} = (4000)^2$$

$$\therefore C = \frac{1}{(16 \times 10^6)(5)} = 12.5 \text{ nF}$$

$$\frac{1}{2RC} = 4000$$

$$\therefore R = \frac{10^9}{(8000)(12.5)} = 10 \text{ k}\Omega$$

$$v(0) = D_2 = 25 \text{ V}$$

$$i_R(0) = \frac{25}{10} = 2.5 \text{ mA}$$

$$i_C(0) = -2.5 - 5 = -7.5 \text{ mA}$$

$$\frac{dv}{dt}(0) = D_1 - 4000D_2 = \frac{-7.5 \times 10^{-3}}{12.5 \times 10^{-9}} = -6 \times 10^5$$

$$\therefore D_1 = -6 \times 10^5 + 4000(25) = -5 \times 10^5 \text{ V/s}$$

$$\text{[b]} \quad v = -5 \times 10^5 t e^{-4000t} + 25e^{-4000t}$$

$$\frac{dv}{dt} = [20 \times 10^8 t - 6 \times 10^5] e^{-4000t}$$

$$i_C = C \frac{dv}{dt} = 12.5 \times 10^{-9} [20 \times 10^8 t - 6 \times 10^5] e^{-4000t}$$

$$= (25,000t - 7.5) e^{-4000t} \text{ mA}, \quad t > 0$$

$$\text{P 8.6 [a]} \quad i_R(0) = \frac{90}{2000} = 45 \text{ mA}$$

$$i_L(0) = -30 \text{ mA}$$

$$i_C(0) = -i_L(0) - i_R(0) = 30 - 45 = -15 \text{ mA}$$

$$\text{[b]} \quad \alpha = \frac{1}{2RC} = \frac{10^9}{(4000)(10)} = 25,000$$

$$\omega_o^2 = \frac{1}{LC} = \frac{(10^3)(10^9)}{(250)(10)} = 4 \times 10^8$$

$$s_{1,2} = -25,000 \pm \sqrt{6.25 \times 10^8 - 10^8(4)} = -25,000 \pm 15,000$$

$$s_1 = -10,000 \text{ rad/s}; \quad s_2 = -40,000 \text{ rad/s}$$

$$v = A_1 e^{-10,000t} + A_2 e^{-40,000t}$$

$$v(0) = A_1 + A_2 = 90$$

$$\frac{dv}{dt}(0) = -10^4 A_1 - 4A_2 \times 10^4 = \frac{-15 \times 10^{-3}}{10 \times 10^{-9}} = -1.5 \times 10^6 \text{ V/s}$$

$$-A_1 - 4A_2 = -150$$

$$\therefore -3A_2 = -60; \quad A_2 = 20; \quad A_1 = 70$$

$$v = 70e^{-10,000t} + 20e^{-40,000t} \text{ V}, \quad t \geq 0$$


$$\text{[c]} \quad i_C = C \frac{dv}{dt}$$

$$= 10 \times 10^{-9} [-70 \times 10^4 e^{-10,000t} - 80 \times 10^4 e^{-40,000t}]$$

$$= -7e^{-10,000t} - 8e^{-40,000t} \text{ mA}$$

$$i_R = 35e^{-10,000t} + 10e^{-40,000t} \text{ mA}$$

$$i_L = -i_C - i_R = -28e^{-10,000t} - 2e^{-40,000t} \text{ mA}, \quad t \geq 0$$

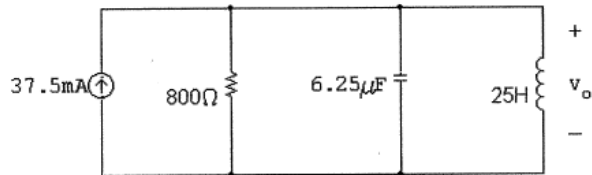P 8.30 For  $t > 0$ 

$$\alpha = \frac{1}{2RC} = 100; \quad \frac{1}{LC} = 6400$$

$$s_{1,2} = -100 \pm 60$$

$$s_1 = -40 \text{ rad/s}; \quad s_2 = -160 \text{ rad/s}$$

$$v_o = V_f + A'_1 e^{-40t} + A'_2 e^{-160t}$$

$$V_f = 0; \quad v_o(0^+) = 0; \quad i_C(0^+) = 37.5 \text{ mA}$$

$$\therefore A'_1 + A'_2 = 0$$

$$\frac{dv_o(0^+)}{dt} = \frac{i_C(0^+)}{6.25 \times 10^{-6}} = 6000 \text{ V/s}$$

$$\frac{dv_o(0^+)}{dt} = -40A'_1 - 160A'_2$$


$$-40A'_1 - 160A'_2 = 6000$$

$$A'_1 + 4A'_2 = -150$$


$$A'_1 + A'_2 = 0$$

$$\therefore A'_1 = 50 \text{ V}; \quad A'_2 = -50 \text{ V}$$

$$v_o = 50e^{-40t} - 50e^{-160t} \text{ V}, \quad t \geq 0$$

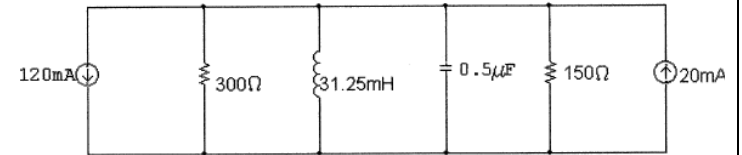P 8.35  $t < 0$ :  $i_L = 3/150 = 20 \text{ mA}$   
 $t > 0$ :

$$300 \parallel 150 = 100 \Omega$$

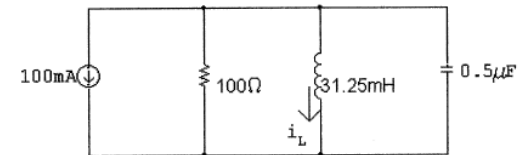

$$i_L(0) = 20 \text{ mA}, \quad i_L(\infty) = -100 \text{ mA}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(31.25)(0.5)} = 64 \times 10^6; \quad \omega_o = 8000 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{10^6}{(200)(0.5)} = 10^4; \quad \alpha^2 = 100 \times 10^6$$

$$\alpha^2 - \omega_o^2 = (100 - 64)10^6 = 36 \times 10^6$$

$$s_{1,2} = -10,000 \pm 6000$$

$$s_1 = -4000 \text{ rad/s}; \quad s_2 = -16,000 \text{ rad/s}$$

$$i_L = I_f + A'_1 e^{-4000t} + A'_2 e^{-16,000t}$$

$$i_L(\infty) = I_f = -100 \text{ mA}$$

$$i_L(0) = A'_1 + A'_2 + I_f = 20 \text{ mA}$$

P 8.38  $\alpha = 800 \text{ rad/s}; \quad \omega_d = 600 \text{ rad/s}$


$$\omega_o^2 - \alpha^2 = 36 \times 10^4; \quad \omega_o^2 = 100 \times 10^4; \quad \omega_o = 1000 \text{ rad/s}$$

$$\alpha = \frac{R}{2L} = 800; \quad R = 1600L$$

$$\frac{1}{LC} = 100 \times 10^4; \quad L = \frac{10^6}{(100 \times 10^4)(500)} = 2 \text{ mH}$$

$$\therefore R = 3.2 \Omega$$
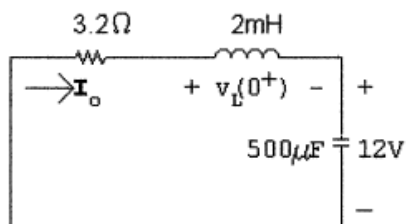
$$i(0^+) = B_1 = 0 \text{ A}; \quad \text{at } t = 0^+$$



$$12 + 0 + v_L(0^+) = 0; \quad v_L(0^+) = -12 \text{ V}$$

$$\frac{di(0^+)}{dt} = \frac{-12}{0.002} = -6000 \text{ A/s}$$

$$\therefore \frac{di(0^+)}{dt} = 600B_2 - 800B_1 = -6000$$

$$\therefore 600B_2 = 800B_1 - 6000; \quad \therefore B_2 = -10 \text{ A}$$

$$\therefore i = -10e^{-800t} \sin 600t \text{ A}, \quad t \geq 0$$

P 8.40 [a]  $t < 0$ :

$$i_o = \frac{120}{8000} = 15 \text{ mA}; \quad v_o = (5000)(0.015) = 75 \text{ V}$$

$t > 0$ :

$$\alpha = \frac{R}{2L} = \frac{5000}{2(1)} = 2500 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(1)(250)} = 4 \times 10^6 = 400 \times 10^4$$

$$\alpha^2 - \omega_o^2 = 625 \times 10^4 - 400 \times 10^4 = 225 \times 10^4$$

$$\therefore s_{1,2} = -2500 \pm 1500$$

$$s_1 = -1000 \text{ rad/s} \quad s_2 = -4000 \text{ rad/s}$$

$$\therefore i_o(t) = A_1 e^{-1000t} + A_2 e^{-4000t}$$

$$i_o(0) = A_1 + A_2 = 15 \times 10^{-3}$$

$$\frac{di_o}{dt}(0) = -1000A_1 - 4000A_2 = 0$$

$$\text{Solving, } A_1 = 20 \text{ mA}; \quad A_2 = -5 \text{ mA}$$

$$i_o(t) = 20e^{-1000t} - 5e^{-4000t} \text{ mA}, \quad t \geq 0^+$$

[b]  $v_o(t) = A_1 e^{-1000t} + A_2 e^{-4000t}$

$$v_o(0) = A_1 + A_2 = 75$$

$$\frac{dv_o}{dt}(0) = -1000A_1 - 4000A_2 = \frac{-15 \times 10^{-3}}{250 \times 10^{-9}}$$

$$\text{Solving, } A_1 = 80 \text{ V}; \quad A_2 = -5 \text{ V}$$

$$v_o(t) = 80e^{-1000t} - 5e^{-4000t} \text{ V}, \quad t \geq 0^+$$


Check:

$$5000i_o + 1 \frac{di_o}{dt} = v_o$$

$$5000i_o = 100e^{-1000t} - 25e^{-4000t}$$


$$\frac{di_o}{dt} = -20e^{-1000t} + 20e^{-4000t}$$

$$\therefore 5000i_o + \frac{di_o}{dt} = 80e^{-1000t} - 5e^{-4000t} \text{ V} \quad (\text{checks})$$

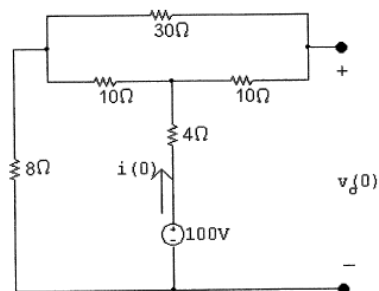P 8.44  $t < 0$ :

$$i(0) = \frac{100}{4 + 8 + 8} = \frac{100}{20} = 5 \text{ A}$$

$$v_o(0) = 100 - 5(4) - 10(5) \left(\frac{10}{50}\right) = 70 \text{ V}$$

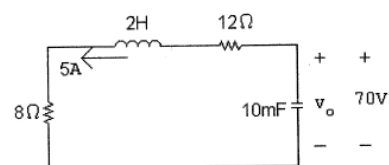 $t > 0$ :

$$\alpha = \frac{R}{2L} = \frac{20}{4} = 5, \quad \alpha^2 = 25$$

$$\omega_o^2 = \frac{1}{LC} = \frac{100}{2} = 50$$

$$\omega_o^2 > \alpha^2 \text{ underdamped}$$

$$v_o = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t; \quad \omega_d = \sqrt{50 - 25} = 5$$

$$v_o = B_1 e^{-5t} \cos 5t + B_2 e^{-5t} \sin 5t$$


$$v_o(0) = B_1 = 70 \text{ V}$$

$$C \frac{dv_o}{dt}(0) = -5, \quad \frac{dv_o}{dt} = \frac{-5}{10} \times 10^3 = -500 \text{ V/s}$$

$$\frac{dv_o}{dt}(0) = -5B_1 + 5B_2 = -500$$


$$5B_2 = -500 + 5B_1 = -500 + 350; \quad B_2 = -150/5 = -30 \text{ V}$$

$$\therefore v_o = 70e^{-5t} \cos 5t - 30e^{-5t} \sin 5t \text{ V}, \quad t \geq 0$$

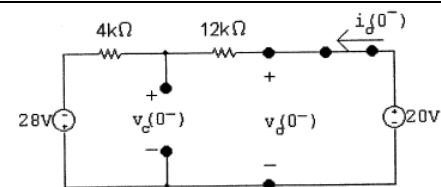P 8.51 [a]  $t < 0$ :

$$i_o(0^-) = \frac{48}{16,000} = 3 \text{ mA}$$

$$v_C(0^-) = 20 - (12,000)(0.003) = -16 \text{ V}$$

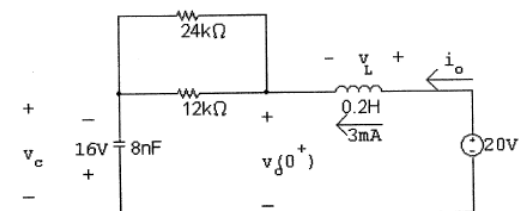 $t = 0^+$ :

$$12 \text{ k}\Omega \parallel 24 \text{ k}\Omega = 8 \text{ k}\Omega$$

$$\therefore v_o(0^+) = (0.003)(8000) - 16 = 24 - 16 = 8 \text{ V}$$

$$\text{and } v_L(0^+) = 20 - 8 = 12 \text{ V}$$

$$[b] v_o(t) = 8000i_o + v_C$$

$$\frac{dv_o}{dt}(t) = 8000 \frac{di_o}{dt} + \frac{dv_C}{dt}$$

$$\frac{dv_o}{dt}(0^+) = 8000 \frac{di_o}{dt}(0^+) + \frac{dv_C}{dt}(0^+)$$

$$v_L(0^+) = L \frac{di_o}{dt}(0^+)$$

$$\frac{di_o}{dt}(0^+) = \frac{v_L(0^+)}{L} = \frac{12}{0.2} = 60 \text{ A/s}$$

$$C \frac{dv_C}{dt}(0^+) = i_o(0^+)$$

$$\therefore \frac{dv_C}{dt}(0^+) = \frac{3 \times 10^{-3}}{8 \times 10^{-9}} = 375,000$$

$$\therefore \frac{dv_o}{dt}(0^+) = 8000(60) + 375,000 = 855,000 \text{ V/s}$$

8.51 (continued)

$$[c] \omega_o^2 = \frac{1}{LC} = \frac{10^9}{1.6} = 625 \times 10^6; \quad \omega_o = 25,000 \text{ rad/s}$$

$$\alpha = \frac{R}{2L} = \frac{8000}{0.4} = 20,000 \text{ rad/s}; \quad \alpha^2 = 400 \times 10^6$$

$$\alpha^2 < \omega_o^2 \quad \text{underdamped}$$

$$s_{1,2} = -20,000 \pm j15,000 \text{ rad/s}$$

$$v_o(t) = V_f + B'_1 e^{-20,000t} \cos 15,000t + B'_2 e^{-20,000t} \sin 15,000t$$

$$V_f = v_o(\infty) = 20 \text{ V}$$

$$8 = 20 + B'_1; \quad B'_1 = -12 \text{ V}$$

$$-20,000B'_1 + 15,000B'_2 = 855,000$$

$$\text{Solving,} \quad B'_2 = 41 \text{ V}$$

$$\therefore v_o(t) = 20 - 12e^{-20,000t} \cos 15,000t + 41e^{-20,000t} \sin 15,000t \text{ V}, \quad t \geq 0^+$$

- 2) Graph the following responses using MathCAD, MatLab, or Excel and turn in printouts of each graph. Include a title that identifies the problem number and indicates whether the graph is overdamped, underdamped, or critically damped. Graph each response from 0 to 5Tau and use good rules for graphing, including a sufficient number of points so that each graph is smooth.

A)  $i(t) = 20e^{-100t} + 30e^{-500t} \text{ A}, t \geq 0$

B)  $i(t) = 20e^{-5,000t} - 30e^{-20,000t} \text{ A}, t \geq 0$

C)  $i(t) = (20,000t + 2)e^{-400t} \text{ A}, t \geq 0$

D)  $i(t) = e^{-10,000t} [30\cos(4000\pi t) + 40\cos(4000\pi t)] \text{ A}, t \geq 0$

E)  $i(t) = e^{-2,500t} [30\cos(4000\pi t) + 40\cos(4000\pi t)] \text{ A}, t \geq 0$

F)  $i(t) = e^{-500t} [30\cos(4000\pi t) + 40\cos(4000\pi t)] \text{ A}, t \geq 0$

```

% EGR 260 - Circuit Analysis
% Solution to Homework #8
% Part 2A _____
t=0.0:0.0005:0.05; % 101 points
iA = 20*exp(-100*t)+20*exp(-500*t);
figure (1)
plot(t,iA)
title('Part 2A - Overdamped')
xlabel('time, t (s)')
ylabel('current, iA (A)')
% Part 2B _____
t=0.0:0.000025:0.0025; % 101 points
iB = 20*exp(-5000*t)-20*exp(-20000*t);
figure (2)
plot(t,iB)
title('Part 2B - Overdamped')
xlabel('time, t (s)')
ylabel('current, iB (A)')
% Part 2C _____
t=0.0:0.000125:0.0125; % 101 points
iC = (20000*t+2).*exp(-400*t);
figure (3)
plot(t,iC)
title('Part 2C - Critically Damped')
xlabel('time, t (s)')
ylabel('current, iC (A)')

```

```

% Part 2D _____
t=0.0:0.000005:0.0005; % 101 points
iD = exp(-10000*t).*(30*cos(4000*pi*t) + 40*sin(4000*pi*t));
figure (4)
plot(t,iD)
title('Part 2D - Underdamped')
xlabel('time, t (s)')
ylabel('current, iD (A)')
% Part 2E _____
t=0.0:0.00002:0.002; % 101 points
iE = exp(-2500*t).*(30*cos(4000*pi*t) + 40*sin(4000*pi*t));
figure (5)
plot(t,iE)
title('Part 2E - Underdamped')
xlabel('time, t (s)')
ylabel('current, iE (A)')
% Part 2F _____
t=0.0:0.00001:0.01; % 101 points
iF = exp(-500*t).*(30*cos(4000*pi*t) + 40*sin(4000*pi*t));
figure (6)
plot(t,iF)
title('Part 2F - Underdamped')
xlabel('time, t (s)')
ylabel('current, iF (A)')

```

