

Solution to Homework Assignment #1

Problem Assignment:

- 1) Chapter 1 # 9, 11, 12, 15, 16, 17, 19, 20, 22, 28, 30
- 2) Using the power rating values from Table 1 (or from the Lecture #2 notes), calculate the following if the cost of electricity is \$0.08/kW·h:
 - A) The cost to run an air conditioner 12 h/day for 30 days
 - B) The cost to watch a television for 4 h/day for 1 year
 - C) The cost to dry your hair with a blow dryer (10 minutes)

Solutions:

P 1.9 First we use Eq. (1.2) to relate current and charge:

$$i = \frac{dq}{dt} = 24 \cos 4000t$$

Therefore, $dq = 24 \cos 4000t dt$

To find the charge, we can integrate both sides of the last equation. Note that we substitute x for q on the left side of the integral, and y for t on the right side of the integral:

$$\int_{q(0)}^{q(t)} dx = 24 \int_0^t \cos 4000y dy$$

We solve the integral and make the substitutions for the limits of the integral, remembering that $\sin 0 = 0$:

$$q(t) - q(0) = 24 \frac{\sin 4000y}{4000} \Big|_0^t = \frac{24}{4000} \sin 4000t - \frac{24}{4000} \sin 4000(0) = \frac{24}{4000} \sin 4000t$$

But $q(0) = 0$ by hypothesis, i.e., the current passes through its maximum value at $t = 0$, so $q(t) = 6 \times 10^{-3} \sin 4000t \text{ C} = 6 \sin 4000t \text{ mC}$

$$\text{P 1.11 } p = (9)(100 \times 10^{-3}) = 0.9 \text{ W}; \quad 5 \text{ hr} \cdot \frac{3600 \text{ s}}{1 \text{ hr}} = 18,000 \text{ s}$$

$$w(t) = \int_0^t p dt \quad w(18,000) = \int_0^{18,000} 0.9 dt = 0.9(18,000) = 16.2 \text{ kJ}$$

P 1.12 Assume we are standing at box A looking toward box B. Then, using the passive sign convention $p = vi$, since the current i is flowing into the + terminal of the voltage v . Now we just substitute the values for v and i into the equation for power. Remember that if the power is positive, B is absorbing power, so the power must be flowing from A to B. If the power is negative, B is generating power so the power must be flowing from B to A.

$$\text{[a]} \quad p = (120)(5) = 600 \text{ W} \quad 600 \text{ W from A to B}$$

$$\text{[b]} \quad p = (250)(-8) = -2000 \text{ W} \quad 2000 \text{ W from B to A}$$

$$\text{[c]} \quad p = (-150)(16) = -2400 \text{ W} \quad 2400 \text{ W from B to A}$$

$$\text{[d]} \quad p = (-480)(-10) = 4800 \text{ W} \quad 4800 \text{ W from A to B}$$

P 1.15 [a] In Car A, the current i is in the direction of the voltage drop across the 12 V battery (the current i flows into the + terminal of the battery of Car A). Therefore using the passive sign convention,

$$p = vi = (30)(12) = 360 \text{ W}.$$

Since the power is positive, the battery in Car A is absorbing power, so Car A must have the "dead" battery.


$$\text{[b]} \quad w(t) = \int_0^t p \, dx; \quad 1 \text{ min} = 60 \text{ s}$$

$$w(60) = \int_0^{60} 360 \, dx$$

$$w = 360(60 - 0) = 360(60) = 21,600 \text{ J} = 21.6 \text{ kJ}$$

$$\text{P 1.16} \quad p = vi; \quad w = \int_0^t p \, dx$$

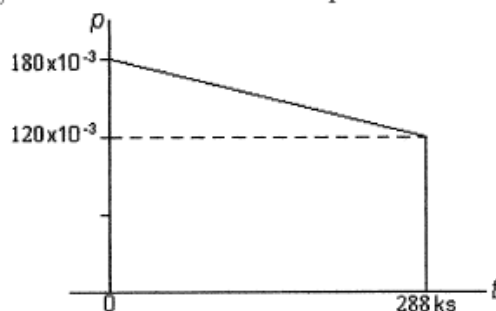Since the energy is the area under the power vs. time plot, let us plot p vs. t .



Note that in constructing the plot above, we used the fact that 80 hr = 288,000 s = 288 ks

$$p(0) = (9)(20 \times 10^{-3}) = 180 \times 10^{-3} \text{ W}$$

$$p(288 \text{ ks}) = (6)(20 \times 10^{-3}) = 120 \times 10^{-3} \text{ W}$$

$$w = (120 \times 10^{-3})(288 \times 10^3) + \frac{1}{2}(180 \times 10^{-3} - 120 \times 10^{-3})(288 \times 10^3) = 43.2 \text{ kJ}$$

P 1.17 [a] $p = vi = 30e^{-500t} - 30e^{-1500t} - 40e^{-1000t} + 50e^{-2000t} - 10e^{-3000t}$
 $p(1 \text{ ms}) = 3.1 \text{ mW}$

[b] $w(t) = \int_0^t (30e^{-500x} - 30e^{-1500x} - 40e^{-1000x} + 50e^{-2000x} - 10e^{-3000x}) dx$
 $= 21.67 - 60e^{-500t} + 20e^{-1500t} + 40e^{-1000t} - 25e^{-2000t} + 3.33e^{-3000t} \mu\text{J}$
 $w(1 \text{ ms}) = 1.24 \mu\text{J}$

[c] $w_{\text{total}} = 21.67 \mu\text{J}$

P 1.19 [a] $0 \text{ s} \leq t < 4 \text{ s}$:

$v = 2.5t \text{ V}; \quad i = 1 \mu\text{A}; \quad p = 2.5t \mu\text{W}$

$4 \text{ s} < t \leq 8 \text{ s}$:

$v = 10 \text{ V}; \quad i = 0 \text{ A}; \quad p = 0 \text{ W}$

$8 \text{ s} \leq t < 16 \text{ s}$:

$v = -2.5t + 30 \text{ V}; \quad i = -1 \mu\text{A}; \quad p = 2.5t - 30 \mu\text{W}$

$16 \text{ s} < t \leq 20 \text{ s}$:

$v = -10 \text{ V}; \quad i = 0 \text{ A}; \quad p = 0 \text{ W}$

$20 \text{ s} \leq t < 36 \text{ s}$:

$v = t - 30 \text{ V}; \quad i = 0.4 \mu\text{A}; \quad p = 0.4t - 12 \mu\text{W}$

$36 \text{ s} < t \leq 46 \text{ s}$:


$v = 6 \text{ V}; \quad i = 0 \text{ A}; \quad p = 0 \text{ W}$

$46 \text{ s} \leq t < 50 \text{ s}$:

$v = -1.5t + 75 \text{ V}; \quad i = -0.6 \mu\text{A}; \quad p = 0.9t - 45 \mu\text{W}$

$t > 50 \text{ s}$:

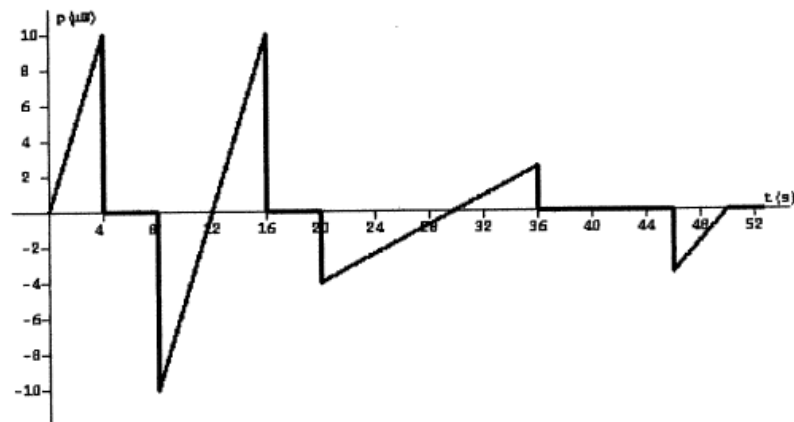$v = 0 \text{ V}; \quad i = 0 \text{ A}; \quad p = 0 \text{ W}$



[b] Calculate the area under the curve from zero up to the desired time:

$$w(4) = \frac{1}{2}(4)(10) = 20 \mu\text{J}$$

$$w(12) = w(4) - \frac{1}{2}(4)(10) = 0 \text{ J}$$

$$w(36) = w(12) + \frac{1}{2}(4)(10) - \frac{1}{2}(10)(4) + \frac{1}{2}(6)(2.4) = 7.2 \mu\text{J}$$

$$w(50) = w(36) - \frac{1}{2}(4)(3.6) = 0 \text{ J}$$

P 1.20 [a] $p = vi = (0.05e^{-1000t})(75 - 75e^{-1000t}) = (3.75e^{-1000t} - 3.75e^{-2000t}) \text{ W}$

$$\frac{dp}{dt} = -3750e^{-1000t} + 7500e^{-2000t} = 0 \quad \text{so} \quad 2e^{-2000t} = e^{-1000t}$$

$$2 = e^{1000t} \quad \text{so} \quad \ln 2 = 1000t \quad \text{thus} \quad p \text{ is maximum at } t = 693.15 \mu\text{s}$$

$$p_{\max} = p(693.15 \mu\text{s}) = 937.5 \text{ mW}$$

$$\begin{aligned} \text{[b]} \quad w &= \int_0^{\infty} [3.75e^{-1000t} - 3.75e^{-2000t}] dt = \left[\frac{3.75}{-1000}e^{-1000t} - \frac{3.75}{-2000}e^{-2000t} \right]_0^{\infty} \\ &= \frac{3.75}{1000} - \frac{3.75}{2000} = 1.875 \text{ mJ} \end{aligned}$$

P 1.22 [a] q = area under i vs. t plot

$$\begin{aligned} &= \left[\frac{1}{2}(5)(4) + (10)(4) + \frac{1}{2}(8)(4) + (8)(6) + \frac{1}{2}(3)(6) \right] \times 10^3 \\ &= [10 + 40 + 16 + 48 + 9]10^3 = 123,000 \text{ C} \end{aligned}$$

[b] $w = \int p dt = \int vi dt$

$$v = 0.2 \times 10^{-3}t + 9 \quad 0 \leq t \leq 15 \text{ ks}$$

$$0 \leq t \leq 4000 \text{ s}$$

$$i = 15 - 1.25 \times 10^{-3}t$$

$$p = 135 - 8.25 \times 10^{-3}t - 0.25 \times 10^{-6}t^2$$

$$\begin{aligned} w_1 &= \int_0^{4000} (135 - 8.25 \times 10^{-3}t - 0.25 \times 10^{-6}t^2) dt \\ &= (540 - 66 - 5.3333)10^3 = 468.667 \text{ kJ} \end{aligned}$$

$$4000 \leq t \leq 12,000$$

$$i = 12 - 0.5 \times 10^{-3}t$$

$$p = 108 - 2.1 \times 10^{-3}t - 0.1 \times 10^{-6}t^2$$

$$\begin{aligned} w_2 &= \int_{4000}^{12,000} (108 - 2.1 \times 10^{-3}t - 0.1 \times 10^{-6}t^2) dt \\ &= (864 - 134.4 - 55.467)10^3 = 674.133 \text{ kJ} \end{aligned}$$

$$12,000 \leq t \leq 15,000$$

$$i = 30 - 2 \times 10^{-3}t$$

$$p = 270 - 12 \times 10^{-3}t - 0.4 \times 10^{-6}t^2$$

$$\begin{aligned} w_3 &= \int_{12,000}^{15,000} (270 - 12 \times 10^{-3}t - 0.4 \times 10^{-6}t^2) dt \\ &= (810 - 486 - 219.6)10^3 = 104.4 \text{ kJ} \end{aligned}$$

$$w_T = w_1 + w_2 + w_3 = 468.667 + 674.133 + 104.4 = 1247.2 \text{ kJ}$$

2A) Since power is constant, $W = P \cdot t = (860 \text{ W})(12 \text{ h/day})(30 \text{ days}) = 309.6 \text{ kW}\cdot\text{h}$
Cost = $(309.6 \text{ kW}\cdot\text{h})(\$0.08/\text{kW}\cdot\text{h}) = \24.77

\$2B) Since power is constant, $W = P \cdot t = (150 \text{ W})(4 \text{ h/day})(365 \text{ days}) = 219 \text{ kW}\cdot\text{h}$
Cost = $(219 \text{ kW}\cdot\text{h})(\$0.08/\text{kW}\cdot\text{h}) = \17.52

2C) Since power is constant, $W = P \cdot t = (1300 \text{ W})(10 \text{ min})(1 \text{ h}/60 \text{ min}) = 0.2667 \text{ kW}\cdot\text{h}$
Cost = $(0.2667 \text{ kW}\cdot\text{h})(\$0.08/\text{kW}\cdot\text{h}) = \0.017

P 1.28

$$p_a = -v_a i_a = -(36)(250 \times 10^{-6}) = -9 \text{ mW}$$

$$p_b = v_b i_b = (44)(-250 \times 10^{-6}) = -11 \text{ mW}$$

$$p_c = v_c i_c = (28)(-250 \times 10^{-6}) = -7 \text{ mW}$$

$$p_d = v_d i_d = (-108)(100 \times 10^{-6}) = -10.8 \text{ mW}$$

$$p_e = v_e i_e = (-32)(150 \times 10^{-6}) = -4.8 \text{ mW}$$

$$p_f = -v_f i_f = -(60)(-350 \times 10^{-6}) = 21 \text{ mW}$$

$$p_g = v_g i_g = (-48)(-200 \times 10^{-6}) = 9.6 \text{ mW}$$

$$p_h = v_h i_h = (80)(-150 \times 10^{-6}) = -12 \text{ mW}$$

$$p_j = -v_j i_j = -(80)(-300 \times 10^{-6}) = 24 \text{ mW}$$

Therefore,

$$\sum P_{\text{abs}} = 21 + 9.6 + 24 = 54.6 \text{ mW}$$

$$\sum P_{\text{del}} = 9 + 11 + 7 + 10.8 + 4.8 + 12 = 54.6 \text{ W}$$

$$\sum P_{\text{abs}} = \sum P_{\text{del}}$$

Thus, the interconnection satisfies the power check

P 1.30 [a] From an examination of reference polarities, elements a , b , e , and f absorb power, while elements c , d , g , and h supply power.

[b]

$$p_a = v_a i_a = (0.300)(25 \times 10^{-6}) = 7.5 \mu\text{W}$$

$$p_b = -v_b i_b = -(-0.100)(10 \times 10^{-6}) = 1 \mu\text{W}$$

$$p_c = v_c i_c = (-0.200)(15 \times 10^{-6}) = -3 \mu\text{W}$$

$$p_d = -v_d i_d = -(-0.200)(-35 \times 10^{-6}) = -7 \mu\text{W}$$

$$p_e = -v_e i_e = -(0.350)(-25 \times 10^{-6}) = 8.75 \mu\text{W}$$

$$p_f = v_f i_f = (0.200)(10 \times 10^{-6}) = 2 \mu\text{W}$$

$$p_g = v_g i_g = (-0.250)(35 \times 10^{-6}) = -8.75 \mu\text{W}$$

$$p_h = v_h i_h = (0.050)(-10 \times 10^{-6}) = -0.5 \mu\text{W}$$

$$\sum P_{\text{abs}} = 7.5 + 1 + 8.75 + 2 = 19.25 \mu\text{W}$$

$$\sum P_{\text{del}} = 3 + 7 + 8.75 + 0.5 = 19.25 \mu\text{W}$$

Thus, $19.25 \mu\text{W}$ of power is delivered and $19.25 \mu\text{W}$ of power is absorbed, and the power balances