

## Solution to HW #3 – Simple Resistive Circuits

### Problem Assignment:

Chapter 3 # 9, 10, 22, 23, 25, 27, 28

P 3.9 [a] For circuit (a)

$$R_{ab} = 15 \parallel (18 + 48 \parallel 16) = 10 \Omega$$

For circuit (b)

$$5 \parallel 10 \parallel 15 \parallel 10 \parallel (12 + 18) = 2 \Omega$$

$$16 \parallel (14 + 2) = 8 \Omega$$

$$R_{ab} = 4 + 8 + 12 = 24 \Omega$$

For circuit (c)

$$144 \parallel (4 + 12) = 14.4 \Omega$$

$$14.4 + 5.6 = 20 \Omega$$

$$20 \parallel 12 = 7.5 \Omega$$

$$7.5 + 2.5 = 10 \Omega$$

$$10 \parallel 15 = 6 \Omega$$

$$14 + 6 + 10 = 30 \Omega$$

$$R_{ab} = 30 \parallel 60 = 20 \Omega$$

$$[b] P_a = \frac{20^2}{10} = 40 \text{ W}$$

$$P_b = \frac{144^2}{27} = 768 \text{ W}$$

$$P_c = 5^2(20) = 500 \text{ W}$$

$$P 3.10 \quad R_{eq} = 6 \parallel 30 \parallel 20 = 4 \Omega$$

$$v_{30A} = v_{4\Omega} = (30 \text{ A})(4 \Omega) = 120 \text{ V}$$

Therefore, since the three original resistors are in parallel with the current source:

$$v_{30\Omega} = v_{30A} = 120 \text{ V}$$

$$\text{Thus, } p_{30\Omega} = \frac{v_{30\Omega}^2}{30} = \frac{120^2}{30} = 480 \text{ W}$$

- P 3.22 [a] The equivalent resistance to the right of the 10 kΩ resistor is  $3\text{ k} + 8\text{ k} + [6\text{ k} \parallel (5\text{ k} + 7\text{ k})] = 15\text{ k}\Omega$ . Therefore,

$$i_{10\text{k}} = \frac{15\text{ k} \parallel 10\text{ k}}{10\text{ k}}(0.002) = \frac{6\text{ k}}{10\text{ k}}(0.002) = 1.2\text{ mA}$$

- [b] The voltage drop across the 10 kΩ resistor can be found using Ohm's law:

$$v_{10\text{k}} = (10,000)i_{10\text{k}} = (10,000)(0.0012) = 12\text{ V}$$

- [c] The voltage  $v_{10\text{k}}$  drops across the 3 kΩ resistor, the 8 kΩ resistor and the equivalent resistance of the 6 kΩ and the parallel branch containing the 5 kΩ and 7 kΩ resistors. Thus, using voltage division,

$$v_{6\text{k}} = \frac{6\text{ k} \parallel (5\text{ k} + 7\text{ k})}{3\text{ k} + 8\text{ k} + [6\text{ k} \parallel (5\text{ k} + 7\text{ k})]}(12) = \frac{4}{15}(12) = 3.2\text{ V}$$

- [d] The voltage  $v_{6\text{k}}$  drops across the branch containing the 5 kΩ and 7 kΩ resistors. Thus, using voltage division,

$$v_{5\text{k}} = \frac{5\text{ k}}{5\text{ k} + 7\text{ k}}(3.2) = 1.33\text{ V}$$

- P 3.23 [a] The voltage drop across the 240 Ω resistor is the same as the voltage drop across the parallel combination of the branch containing the 240 Ω resistor and the branch containing the 180 Ω and 300 Ω resistors. Thus by voltage division,

$$v_{240} = \frac{240 \parallel (180 + 300)}{[240 \parallel (180 + 300)] + 140 + 200}(10) = \frac{160}{500}(10) = 3.2\text{ V}$$

- [b] The current in the 240 Ω resistor can be found from its voltage using Ohm's law:

$$i_{240} = \frac{v_{240}}{240} = \frac{3.2}{240} = 13.33\text{ mA}$$

- [c] The current in the 140 Ω resistor divides between two branches – one containing the 180 Ω and 300 Ω resistors and the other containing the 240 Ω resistor. Using current division,

$$i_{240} = \frac{240 \parallel (180 + 300)}{240}(i_{140}) = 0.01333 \quad \text{so} \quad i_{140} = \frac{240(0.01333)}{160} = 20\text{ mA}$$

$$\text{P 3.25 } 60 \parallel 30 = 20 \Omega$$

$$i_{30\Omega} = \frac{(25)(75)}{125} = 15 \text{ A}$$

$$v_2 = (15)(20) = 300 \text{ V}$$

$$v_2 + 30i_{30} = 750 \text{ V}$$

$$v_1 - 12(25) = 750$$

$$v_1 = 1050 \text{ V}$$

$$\text{P 3.27 } 54 \Omega \parallel 27 \Omega = 18 \Omega; \quad 18 \Omega + 2 \Omega = 20 \Omega; \quad 20 \parallel (10 + 15 + 35) = 15 \Omega;$$

$$\text{Therefore, } i_g = \frac{675}{30 + 15} = 15 \text{ A}$$

$$i_{2\Omega} = \frac{20 \parallel 60}{20}(15) = 11.25 \text{ A}; \quad i_o = \frac{27 \parallel 54}{27}(11.25) = 7.5 \text{ A}$$

$$\text{P 3.28 [a] } 40 \parallel 10 = 8 \Omega$$

$$i_{120\text{V}} = \frac{120}{7.5} = 16 \text{ A}$$

$$8 + 2 = 10 \Omega$$

$$i_{4\Omega} = \frac{7.5}{4 + 6}(16) = 12 \text{ A}$$

$$15 \parallel 10 = 6 \Omega$$

$$i_{2\Omega} = \frac{6}{2 + 8}(12) = 7.2 \text{ A}$$

$$6 + 4 = 10 \Omega$$

$$i_o = \frac{8}{40}(7.2) = 1.44 \text{ A}$$

$$30 \parallel 10 = 7.5 \Omega$$

$$\text{[b] } i_{15\Omega} = i_{4\Omega} - i_{2\Omega} = 12 - 7.2 = 4.8 \text{ A}$$

$$P_{15\Omega} = (4.8)^2(15) = 345.6 \text{ W}$$