

EGR 260

Circuit Analysis

File: N260H8BS

Solution to Homework Assignment #8

Chapter 6 in **Electric Circuits, 8th Edition** by Nilsson

Ch. 6 problems: 15, 17, 18, 19, 25, 26, 27

P 6.15 [a] $0 \leq t \leq 100 \mu\text{s}$

$$C = 0.2 \mu\text{F} \quad \frac{1}{C} = 5 \times 10^6$$

$$v = 5 \times 10^6 \int_0^t -0.04 dx + 40$$

$$v = -200 \times 10^3 t + 40 \text{ V} \quad 0 \leq t \leq 100 \mu\text{s}$$

$$v(100 \mu\text{s}) = -20 + 40 = 20 \text{ V}$$

[b] $100 \mu\text{s} \leq t \leq 300 \mu\text{s}$

$$v = 5 \times 10^6 \int_{100 \times 10^{-6}}^t 0.08 dx + 20 = 4 \times 10^5 t - 40 + 20$$

$$v = 4 \times 10^5 t - 20 \text{ V} \quad 100 \leq t \leq 300 \mu\text{s}$$


$$v(300 \mu\text{s}) = 4 \times 10^5 (300 \times 10^{-6}) - 20 = 100 \text{ V}$$

[c] $300 \mu\text{s} \leq t < \infty$

$$v = 5 \times 10^6 \int_{300 \times 10^{-6}}^t 0 dx + 100 = 100$$

$$v = 100 \text{ V}, \quad 300 \mu\text{s} \leq t < \infty$$

[d]

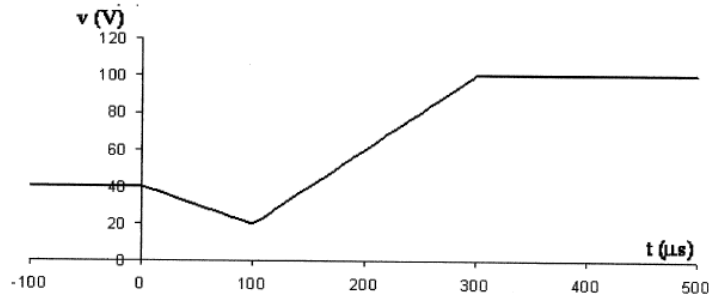

P 6.17 [a] $i = \frac{50 \times 10^{-3}}{10 \times 10^{-6}} t = 5 \times 10^3 t \quad 0 \leq t \leq 10 \mu\text{s}$

$$i = 50 \times 10^{-3} \quad 10 \leq t \leq 30 \mu\text{s}$$

$$q = \int_0^{10 \times 10^{-6}} 5 \times 10^3 t dt + \int_{10 \times 10^{-6}}^{30 \times 10^{-6}} 50 \times 10^{-3} dt$$

$$= 5 \times 10^3 \frac{t^2}{2} \Big|_0^{10 \times 10^{-6}} + 50 \times 10^{-3} (20 \times 10^{-6})$$

$$= 5 \times 10^3 \left(\frac{1}{2}\right) (100 \times 10^{-12}) + 1000 \times 10^{-3} \times 10^{-6}$$

$$= 1.25 \mu\text{C}$$

[b] $i = 200 \times 10^{-3} - 5 \times 10^{-3} t \quad 30 \mu\text{s} \leq t \leq 50 \mu\text{s}$

$$q = 1.25 \times 10^{-6} + \int_{30 \times 10^{-6}}^{50 \times 10^{-6}} [200 \times 10^{-3} - 5 \times 10^3 t] dt$$

$$= 1.25 \times 10^{-6} + 200 \times 10^{-3} (20 \times 10^{-6}) - 5 \times 10^3 \frac{t^2}{2} \Big|_{30 \times 10^{-6}}^{50 \times 10^{-6}}$$

$$= 1.25 \times 10^{-6} + 4000 \times 10^{-9} - 5 \times 10^3 \left[\frac{2500 - 900}{2} \right] 10^{-12}$$

$$= 1.25 \mu\text{C}$$

Since $q = vC$, $\therefore v = 1.25/0.25 = 5 \text{ V}$.

[c] $i = -300 \times 10^{-3} + 5 \times 10^{-3} t \quad 50 \mu\text{s} \leq t \leq 60 \mu\text{s}$

$$q = 1.25 \times 10^{-6} + \int_{50 \times 10^{-6}}^{60 \times 10^{-6}} [-300 \times 10^{-3} + 5 \times 10^3 t] dt$$

$$= 1.25 \times 10^{-6} - 300 \times 10^{-3} (10 \times 10^{-6})$$

$$+ 5 \times 10^3 \left[\frac{3600 - 2500}{2} \right] 10^{-12}$$

$$= 1 \mu\text{C}$$

$$v = \frac{1 \times 10^{-6}}{0.25 \times 10^{-6}} = 4 \text{ V}$$

$$w = \frac{C}{2} v^2 = \frac{1}{2} (0.25) \times 10^{-6} (16) = 2 \mu\text{J}$$

P 6.18 [a] $v = 5 \times 10^6 \int_0^{250 \times 10^{-6}} 100 \times 10^{-3} e^{-1000t} dt - 60.6$

$$= 500 \times 10^3 \left. \frac{e^{-1000t}}{-1000} \right|_0^{250 \times 10^{-6}} - 60.6$$

$$= 500(1 - e^{-0.25}) - 60.6 = 50 \text{ V}$$

$$w = \frac{1}{2} C v^2 = \frac{1}{2} (0.2) (10^{-6}) (50)^2 = 250 \mu\text{J}$$

[b] $v = 500 - 60.6 = 439.40 \text{ V}$

$$w = \frac{1}{2} (0.2) \times 10^{-6} (439.40)^2 = 19.31 \text{ mJ} = 19,307.24 \mu\text{J}$$

P 6.19 [a] $w(0) = \frac{1}{2} C [v(0)]^2 = \frac{1}{2} (0.40) \times 10^{-6} (25)^2 = 125 \mu\text{J}$

[b] $v = (A_1 t + A_2) e^{-1500t}$

$$v(0) = A_2 = 25 \text{ V}$$

$$\frac{dv}{dt} = -1500 e^{-1500t} (A_1 t + A_2) + e^{-1500t} (A_1)$$

$$= (-1500 A_1 t - 1500 A_2 + A_1) e^{-1500t}$$

$$\frac{dv}{dt}(0) = A_1 - 1500 A_2$$

$$i = C \frac{dv}{dt}, \quad i(0) = C \frac{dv(0)}{dt}$$

$$\therefore \frac{dv(0)}{dt} = \frac{i(0)}{C} = \frac{90 \times 10^{-3}}{0.40 \times 10^{-6}} = 225 \times 10^3$$

$$\therefore 225 \times 10^3 = A_1 - 1500(25)$$

$$\text{Thus, } A_1 = 2.25 \times 10^5 + 3.75 \times 10^4 = 262,500 \frac{\text{V}}{\text{s}}$$

[c] $v = (262,500t + 25) e^{-1500t}$

$$i = C \frac{dv}{dt} = 0.40 \times 10^{-6} \frac{d}{dt} (262,500t + 25) e^{-1500t}$$

$$i = \frac{d}{dt} [(0.105t + 10 \times 10^{-6}) e^{-1500t}]$$

$$= (0.105t + 10 \times 10^{-6}) (-1500) e^{-1500t} + e^{-1500t} (0.105)$$

$$= (-157.5t - 15 \times 10^{-3} + 0.105) e^{-1500t}$$


$$= (0.09 - 157.5t) e^{-1500t} \text{ A}, \quad t \geq 0$$

$$= (90 - 157,500t) e^{-1500t} \text{ mA}, \quad t \geq 0$$

P 6.25 $\frac{1}{21} + \frac{1}{28} = \frac{7}{84} \therefore C_{eq} = 12 \mu F$

$-10V - 5V = -15V$


$24 + 12 = 36 \mu F$

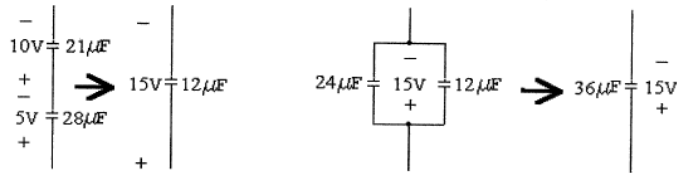

$\frac{1}{36} + \frac{1}{36} = \frac{2}{36} \therefore C_{eq} = 18 \mu F$

$-15V + 2V = -13V$


$12 + 20 = 32 \mu F$

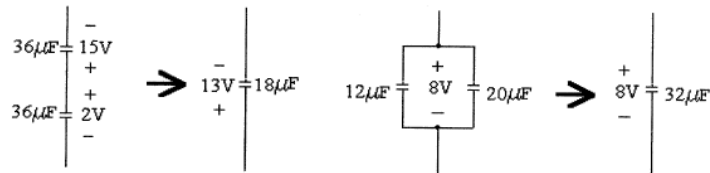

$18 + 14 = 32 \mu F$

$\frac{1}{32} + \frac{1}{32} = \frac{2}{32} \therefore C_{eq} = 16 \mu F$

$8V - 13V = -5V$

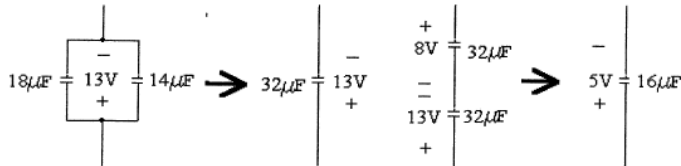




P 6.26 $\frac{1}{C_1} = \frac{1}{8} + \frac{1}{32} = \frac{5}{32}; C_1 = 6.4 \text{ nF}$

$C_2 = 5.6 + 6.4 = 12 \text{ nF}$

$\frac{1}{C_3} = \frac{1}{18} + \frac{1}{12} = \frac{10}{72}; C_3 = 7.2 \text{ nF}$


$C_4 = 12.8 + 7.2 = 20 \text{ nF}$

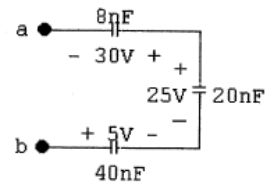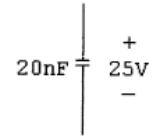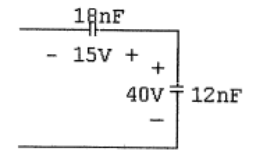$\frac{1}{C_5} = \frac{1}{8} + \frac{1}{20} + \frac{1}{40} = \frac{1}{5}; C_5 = 5 \text{ nF}$



Equivalent capacitance is 5 nF with an initial voltage drop of -10 V.

P 6.27 [a]

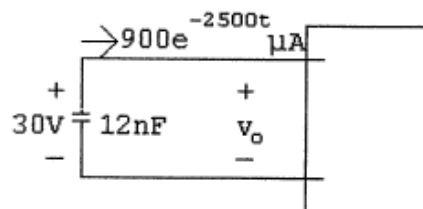

$$\begin{aligned}
 v_o &= -\frac{10^9}{12} \int_0^t 900 \times 10^{-6} e^{-2500x} dx + 30 \\
 &= -75,000 \frac{e^{-2500x}}{-2500} \Big|_0^t + 30 \\
 &= 30e^{-2500t} \text{ V}, \quad t \geq 0
 \end{aligned}$$

$$\begin{aligned}
 \text{[b]} \quad v_1 &= -\frac{10^9}{20} (900 \times 10^{-6}) \frac{e^{-2500x}}{-2500} \Big|_0^t + 45 \\
 &= 18e^{-2500t} + 27 \text{ V}, \quad t \geq 0
 \end{aligned}$$

$$\begin{aligned}
 \text{[c]} \quad v_2 &= -\frac{10^9}{30} (900 \times 10^{-6}) \frac{e^{-2500x}}{-2500} \Big|_0^t - 15 \\
 &= 12e^{-2500t} - 27 \text{ V}, \quad t \geq 0
 \end{aligned}$$

$$\begin{aligned}
 \text{[d]} \quad p &= vi = (30e^{-2500t})(900 \times 10^{-6})e^{-2500t} \\
 &= 27 \times 10^{-3} e^{-5000t} \\
 w &= \int_0^\infty 27 \times 10^{-3} e^{-5000t} dt \\
 &= 27 \times 10^{-3} \frac{e^{-5000t}}{-5000} \Big|_0^\infty \\
 &= -5.4 \times 10^{-6} (0 - 1) = 5.4 \mu\text{J}
 \end{aligned}$$

$$\begin{aligned}
 \text{[e]} \quad w &= \frac{1}{2} (20 \times 10^{-9}) (45)^2 + \frac{1}{2} (30 \times 10^{-9}) (15)^2 \\
 &= 20.25 \times 10^{-6} + 3.375 \times 10^{-6} \\
 &= 23.625 \mu\text{J}
 \end{aligned}$$

$$\text{[f]} \quad w_{\text{trapped}} = w_{\text{initial}} - w_{\text{delivered}} = 23.625 - 5.4 = 18.225 \mu\text{J}$$

$$\begin{aligned}
 \text{[g]} \quad w_{\text{trapped}} &= \frac{1}{2} (20 \times 10^{-9}) (27)^2 + \frac{1}{2} (30 \times 10^{-9}) (27)^2 \\
 &= (10 + 15) (27)^2 \times 10^{-9} \\
 &= 18.225 \mu\text{J}
 \end{aligned}$$

$$\text{CHECK: } 18.225 + 5.4 = 23.625 \mu\text{J}$$