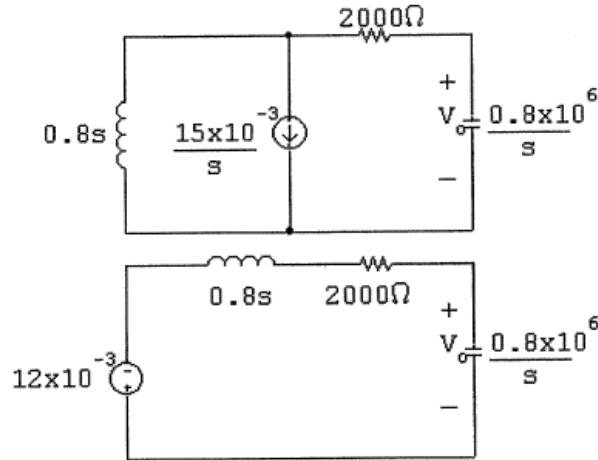


Solution to Homework Assignment #2

1) Work the following problems from Ch. 13 of *Electric Circuits, 8th Edition* by Nilsson: 9, 10, 13, 17, 27(a & c only), 44, 49, 51, 69a

P 13.9 [a] For $t > 0$:



$$\begin{aligned}
 \text{[b]} \quad V_o &= \frac{-12 \times 10^{-3}(0.8/s) \times 10^6}{0.8s + 2000 + (0.8 \times 10^6)/s} \\
 &= \frac{-9600}{0.8s^2 + 2000s + 0.8 \times 10^6} \\
 &= \frac{-12,000}{s^2 + 2500s + 10^6}
 \end{aligned}$$


$$\text{[c]} \quad V_o = \frac{-12,000}{(s + 500)(s + 2000)} = \frac{K_1}{s + 500} + \frac{K_2}{s + 2000}$$

$$K_1 = -8; \quad K_2 = 8$$

$$V_o = \frac{-8}{s + 500} + \frac{8}{s + 2000}$$

$$v_o(t) = (-8e^{-500t} + 8e^{-2000t})u(t) \text{ V}$$

P 13.10 [a] For $t < 0$:

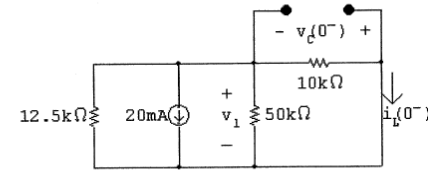


$$\frac{1}{R_e} = \frac{1}{12.5} + \frac{1}{50} + \frac{1}{10} = \frac{1}{5}; \quad R_e = 5 \text{ k}\Omega$$

$$v_1 = -20(5) = -100 \text{ V}$$


$$i_L(0^-) = \frac{-100}{10} \times 10^{-3} = -10 \text{ mA}$$

$$v_C(0^-) = -v_1 = 100 \text{ V}$$

For $t = 0^+$:

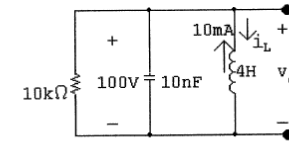

s -domain circuit:

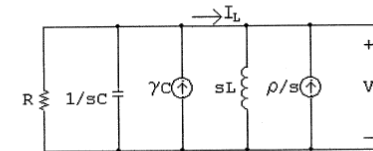

where

$$R = 10 \text{ k}\Omega; \quad C = 10 \text{ nF}; \quad \gamma = 100 \text{ V};$$

$$L = 4 \text{ H}; \quad \text{and} \quad \rho = 10 \text{ mA}$$

$$\text{[b]} \quad \frac{V_o}{R} + V_o sC - \gamma C + \frac{V_o}{sL} - \frac{\rho}{s} = 0$$

$$\therefore V_o = \frac{\gamma[s + (\rho/\gamma C)]}{s^2 + (1/RC)s + (1/LC)}$$

$$\frac{\rho}{\gamma C} = \frac{10 \times 10^{-3}}{(100)(10)10^{-9}} = 10^4$$

$$\frac{1}{RC} = \frac{10^9}{10^5} = 10^4$$

$$\frac{1}{LC} = \frac{10^9}{40} = 25 \times 10^6$$

$$V_o = \frac{100(s + 10^4)}{s^2 + 10^4s + 25 \times 10^6}$$

$$[c] I_L = \frac{V_o}{sL} - \frac{\rho}{s} = \frac{V_o}{4s} - \frac{10 \times 10^{-3}}{s}$$

$$I_L = \frac{25(s + 10^4)}{s(s^2 + 10^4s + 25 \times 10^6)} - \frac{10^{-2}}{s} = \frac{-0.01(s + 7500)}{(s + 5000)^2}$$

$$[d] V_o = \frac{100(s + 10^4)}{s^2 + 10^4s + 25 \times 10^6}$$

$$= \frac{100(s + 10^4)}{(s + 5000)^2} = \frac{K_1}{(s + 5000)^2} + \frac{K_2}{s + 5000}$$

$$K_1 = 100(5000) = 5 \times 10^5$$

$$K_2 = \frac{d}{ds} [100(s + 10,000)]_{s=-5000} = 100$$

$$V_o = \frac{5 \times 10^5}{(s + 5000)^2} + \frac{100}{s + 5000}$$

$$v_o = [5 \times 10^5 t e^{-5000t} + 100 e^{-5000t}] u(t) \text{ V}$$

$$[e] I_L = \frac{-0.01(s + 7500)}{(s + 5000)^2}$$

$$= \frac{K_1}{(s + 5000)^2} + \frac{K_2}{s + 5000}$$


$$K_1 = -0.01(2500) = -25$$

$$K_2 = \frac{d}{ds} [-0.01(s + 7500)]_{s=-5000} = -0.01$$

$$I_L = \left[\frac{-25,000}{(s + 5000)^2} - \frac{10}{s + 5000} \right] \times 10^{-3}$$

$$i_L = -[25,000t + 10] e^{-5000t} u(t) \text{ mA}$$

P 13.13 [a] For $t < 0$:

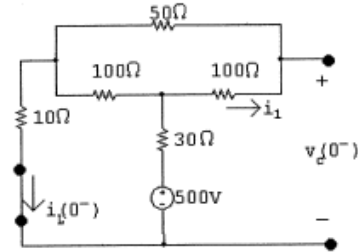


$$i_L(0^-) = \frac{500}{30 + 60 + 10} = 5 \text{ A}$$

$$i_1 = \frac{5(100)}{250} = 2 \text{ A}$$

$$v_c(0^-) = 500 - 5(30) - 2(100) = 500 - 350 = 150 \text{ V}$$

For $t > 0$:

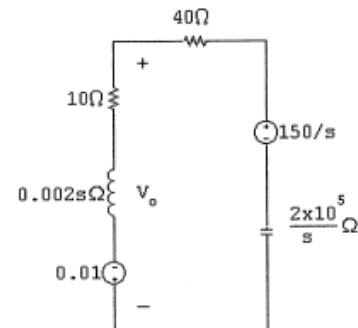

$$[b] \frac{V_o + 0.01}{10 + 0.002s} + \frac{V_o - 150/s}{40 + 2 \times 10^5/s} = 0$$


$$V_o \left[\frac{1}{10 + 0.002s} + \frac{s}{40s + 2 \times 10^5} \right] = \frac{150}{40s + 2 \times 10^5} - \frac{0.01}{10 + 0.002s}$$

$$V_o = \frac{-50(s + 5000)}{s^2 + 25,000s + 10^8} = \frac{-50(s + 5000)}{(s + 5000)(s + 20,000)}$$

$$V_o = \frac{-50}{s + 20,000}$$

$$[c] v_o(t) = -50 e^{-20,000t} u(t) \text{ V}$$

P 13.17

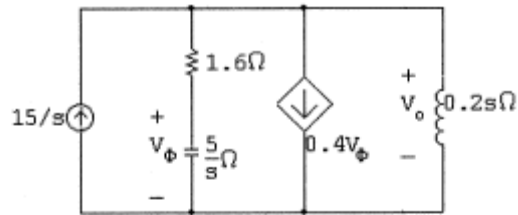

$$\frac{15}{s} = \frac{V_o}{1.6 + 5/s} + 0.4V_\phi + \frac{V_o}{0.2s}$$

$$V_\phi = \frac{5/s}{1.6 + 5/s} V_o = \frac{5V_o}{1.6s + 5}$$

$$\begin{aligned} \therefore \frac{15}{s} &= \frac{V_o s}{1.6s + 5} + \frac{2V_o}{1.6s + 5} + \frac{5V_o}{s} \\ &= V_o \left[\frac{s(s+2) + 5(1.6s+5)}{s(1.6s+5)} \right] \end{aligned}$$

$$15(1.6s + 5) = V_o(s^2 + 10s + 25)$$


$$\therefore V_o = \frac{15(1.6s + 5)}{(s+5)^2} = \frac{K_1}{(s+5)^2} + \frac{K_2}{s+5}$$

$$K_1 = 15(-8 + 5) = -45; \quad K_2 = 24$$

$$V_o = \frac{-45}{(s+5)^2} + \frac{24}{s+5}$$

$$v_o(t) = [-45te^{-5t} + 24e^{-5t}]u(t) \text{ V}$$

P 13.27 [a]

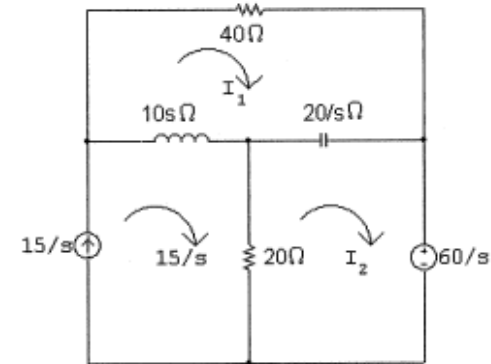

$$40I_1 + \frac{20}{s}(I_1 - I_2) + 10s(I_1 - 15/s) = 0$$

$$20(I_2 - 15/s) + \frac{20}{s}(I_2 - I_1) + \frac{60}{s} = 0$$

or

$$(s^2 + 4s + 2)I_1 - 2I_2 = 15s$$

$$-I_1 + (s+1)I_2 = 12$$

$$\Delta = \begin{vmatrix} (s^2 + 4s + 2) & -2 \\ -1 & (s+1) \end{vmatrix} = s(s+2)(s+3)$$

$$N_1 = \begin{vmatrix} 15s & -2 \\ 12 & (s+1) \end{vmatrix} = 15s^2 + 15s + 24$$

$$I_1 = \frac{N_1}{\Delta} = \frac{15s^2 + 15s + 24}{s(s+2)(s+3)}$$

$$N_2 = \begin{vmatrix} (s^2 + 4s + 2) & 15s \\ -1 & 12 \end{vmatrix} = 12s^2 + 63s + 24$$

$$I_2 = \frac{N_2}{\Delta} = \frac{12s^2 + 63s + 24}{s(s+2)(s+3)}$$


$$[c] I_1 = \frac{4}{s} - \frac{27}{s+2} + \frac{38}{s+3}$$

$$i_1(t) = (4 - 27e^{-2t} + 38e^{-3t})u(t) \text{ A}$$

$$I_2 = \frac{4}{s} + \frac{27}{s+2} - \frac{19}{s+3}$$

$$i_2(t) = (4 + 27e^{-2t} - 19e^{-3t})u(t) \text{ A}$$

P 13.44

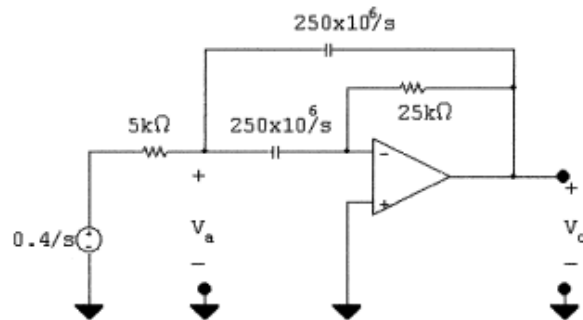

$$\frac{V_a - 0.4/s}{5000} + \frac{V_a s}{250 \times 10^6} + \frac{(V_a - V_o)s}{250 \times 10^6} = 0$$

$$\frac{(0 - V_a)s}{250 \times 10^6} + \frac{(0 - V_o)}{25,000} = 0$$

$$V_a = \frac{-10^4 V_o}{s}$$

$$\therefore V_o(s^2 + 20,000s + 500 \times 10^6) = -20,000$$

$$V_o = \frac{-20,000}{(s + 10,000 - j20,000)(s + 10,000 + j20,000)}$$

$$K_1 = \frac{-20,000}{j40,000} = j0.5 = 0.5 \angle 90^\circ$$

$$v_o(t) = e^{-10,000t} \cos(20,000t + 90^\circ) = -e^{-10,000t} \sin(20,000t)u(t) \text{ V}$$

$$P 13.49 [a] \frac{V_o}{V_i} = \frac{1/sC}{R + 1/sC} = \frac{1}{RCs + 1}$$

$$H(s) = \frac{(1/RC)}{s + (1/RC)} = \frac{50}{s + 50}; \quad -p_1 = -50 \text{ rad/s}$$

$$[b] \frac{V_o}{V_i} = \frac{R}{R + 1/sC} = \frac{RCs}{RCs + 1} = \frac{s}{s + (1/RC)}$$

$$= \frac{s}{s + 50}; \quad z_1 = 0, \quad -p_1 = -50 \text{ rad/s}$$


$$[c] \frac{V_o}{V_i} = \frac{sL}{R + sL} = \frac{s}{s + R/L} = \frac{s}{s + 3 \times 10^6}$$

$$z_1 = 0; \quad -p_1 = -3 \times 10^6 \text{ rad/s}$$

$$[d] \frac{V_o}{V_i} = \frac{R}{R + sL} = \frac{R/L}{s + (R/L)} = \frac{3 \times 10^6}{s + 3 \times 10^6}$$


$$-p_1 = -3 \times 10^6 \text{ rad/s}$$

[e]

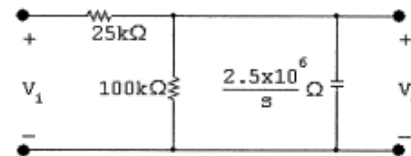

$$\frac{V_o s}{2.5 \times 10^6} + \frac{V_o}{10^5} + \frac{V_o - V_i}{25 \times 10^3} = 0$$

P 13.69 [a]

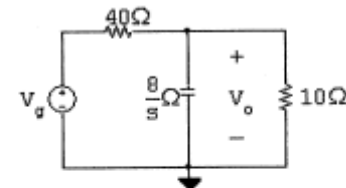


$$\frac{V_o - V_g}{40} + \frac{V_o s}{8} + \frac{V_o}{10} = 0$$

$$(5s + 5)V_o = V_g$$

$$H(s) = \frac{V_o}{V_g} = \frac{0.2}{s + 1}; \quad h(\lambda) = 0.2e^{-\lambda}u(\lambda)$$

P 13.51 [a]

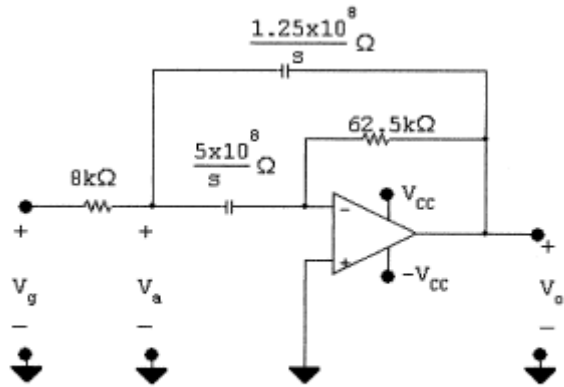

$$\frac{V_a - V_g}{8000} + \frac{V_a s}{5 \times 10^8} + \frac{(V_a - V_o)s}{1.25 \times 10^8} = 0$$

$$\frac{-V_a s}{5 \times 10^8} - \frac{V_o}{62,500} = 0; \quad V_a = \frac{-8000V_o}{s}$$

$$\therefore \frac{-8000V_o}{s}(5s + 62,500) - 4sV_o = 62,500V_g$$

$$\therefore H(s) = \frac{V_o}{V_g} = \frac{-15,625s}{s^2 + 10,000s + 125 \times 10^6}$$

$$s_{1,2} = -5000 \pm \sqrt{25 \times 10^6 - 125 \times 10^6} = -5000 \pm j10,000$$

$$H(s) = \frac{-15,625s}{(s + 5000 - j10,000)(s + 5000 + j10,000)}$$

[b] $-p_1 = -5000 + j10,000$ rad/s

$-p_2 = -5000 - j10,000$ rad/s


$z = 0$

2) Use Laplace transforms to solve problem 7.81 of *Electric Circuits, 8 E* by Nilsson.

7.81 The voltage waveform shown in Fig. P7.81(a) is applied to the circuit of Fig. P7.81(b). The initial voltage on the capacitor is zero.


- Calculate $v_o(t)$.
- Make a sketch of $v_o(t)$ versus t .

Figure P7.81

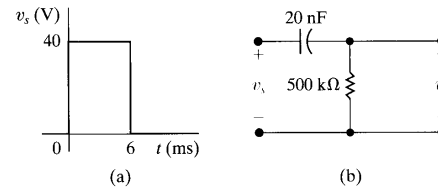

Solution: $v_s(t) = 40[u(t) - u(t-0.006)]$ so $V_s(s) = \frac{40}{s} - \frac{40e^{-0.006s}}{s}$

s-domain circuit:

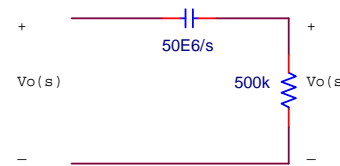

$$V_o(s) = V_s(s) \left[\frac{500k}{500k + \frac{50 \times 10^6}{s}} \right] = V_s(s) \left[\frac{s}{s + 100} \right]$$

$$V_o(s) = \left[\frac{40}{s} - \frac{40e^{-0.006s}}{s} \right] \left[\frac{s}{s + 100} \right] = \frac{40}{s + 100} - \frac{40e^{-0.006s}}{s + 100}$$

$$v_o(t) = 40e^{-100t}u(t) - 40e^{-100(t-0.006)}u(t - 0.006) \text{ V}$$


Sketch:

$$v(0^+) = 40e^0 = 40$$


$$v(6\text{ms}^-) = 40e^{-0.6} - 0 = 21.95$$

$$v(6\text{ms}^+) = 40e^{-0.6} - 40e^0 = -18.05$$
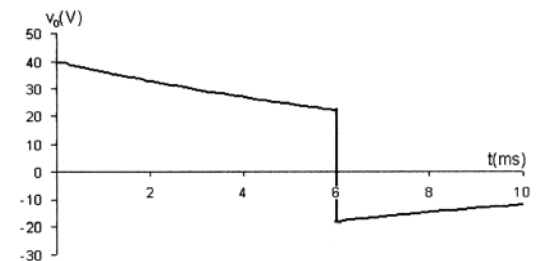
$$v(\infty) = 40e^{-\infty} - 40e^{-\infty} = 0$$



P 13.55 [a]

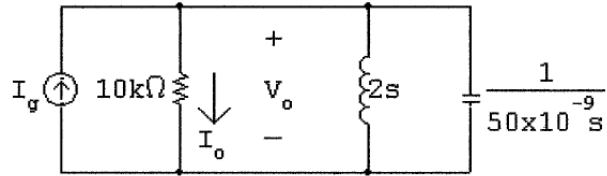

$$\frac{V_o}{10,000} + \frac{V_o}{2s} + V_o(50 \times 10^{-9})s = I_g$$

$$\therefore V_o = \frac{20 \times 10^6 s}{s^2 + 2000s + 10 \times 10^6} \cdot I_g$$

$$I_g = \frac{60 \times 10^{-3} s}{s^2 + 16 \times 10^6}; \quad I_o = \frac{V_o}{10^4}$$

$$\therefore H(s) = \frac{2000s}{s^2 + 2000s + 10^7}$$

3) Work problem 4.4-7 in *Linear Signals & Systems, 2nd Ed.* by Lathi:

4.4-7 Find the output voltage $y(t)$ for the network in Fig. P4.4-7 for the initial conditions $i_L(0) = 1$ A and $v_C(0) = 3$ V.



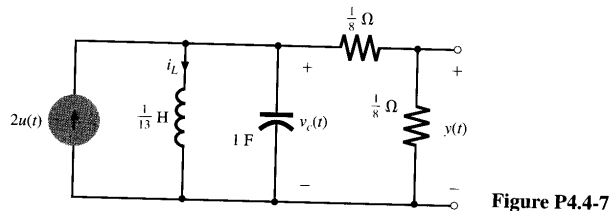
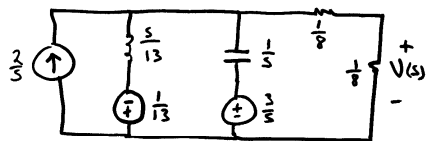


Figure P4.4-7

s-Domain ckt

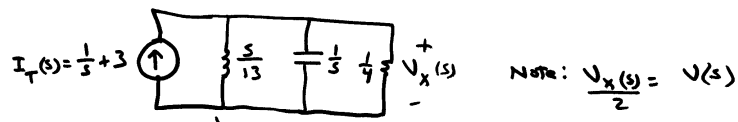

After transforming the voltage sources:

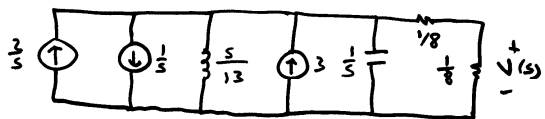

$$Z = \frac{1}{13} \parallel \frac{1}{3} \parallel \frac{1}{8} = \frac{5}{s^2 + 4s + 13}$$

$$V_X(s) = I_T(s) \cdot Z = \left(\frac{1}{3} + 3\right) \left(\frac{5}{s^2 + 4s + 13}\right) = \frac{35 + 1}{s^2 + 4s + 13}$$

$$V_X(s) = \frac{3(s+2)}{(s+2)^2 + 3^2} - \frac{5}{(s+2)^2 + 3^2}$$


$$V_X(s) = e^{-2t} \left[3 \cos(3t) - \frac{5}{3} \sin(3t) \right] u(t)$$

$$V(s) = \frac{V_X}{2} = e^{-2t} \left[1.5 \cos(3t) - \frac{5}{6} \sin(3t) \right] u(t) V$$


$$V(t) = 1.716 e^{-2t} \cos(3t + 29.1^\circ) V = y(t)$$

4) A) Determine the transfer function $H(s) = V(s)/I_g(s)$ for the circuit shown below.

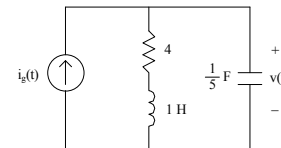B) Determine the impulse response [i.e., find $v(t)$ if $i_g(t) = \delta(t)$ A].
C) Determine the unit step response [i.e., find $v(t)$ if $i_g(t) = u(t)$ A].



A) Assume zero initial conditions

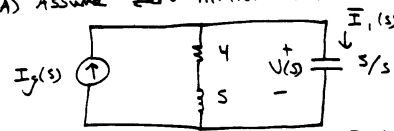

By current division: $I_1(s) = I_g(s) \left[\frac{4+s}{4+s+5s} \right]$

$$V(s) = \frac{5}{s} \cdot I_1(s) = I_g(s) \left(\frac{5}{s} \right) \left[\frac{4+s}{4+s+5s} \right]$$

$$H(s) = \frac{V(s)}{I_g(s)} = \frac{5s+20}{s(s^2+4s+5)} \quad H(s) = \frac{5s+20}{s^2+4s+5}$$

B) $i_g(t) = \delta(t)$ so $I_g(s) = 1$; $V(s) = H(s) I_g(s) = H(s)$

$$v(t) = h(t) = \mathcal{Z}^{-1}\{H(s)\}$$

$H(s)$ has complex poles so

$$H(s) = \frac{5s+20}{(s+2)^2+1^2} = \frac{5(s+2)}{(s+2)^2+1^2} + \frac{10(1)}{(s+2)^2+1^2}$$

so $v(t) = h(t) = \text{impulse response} = e^{-2t} [5 \cos t + 10 \sin t] V$

C) $i_g(t) = u(t)$, so $I_g(s) = 1/s$

$$V(s) = H(s) I_g(s) = \frac{5s+20}{s(s^2+4s+5)} = \frac{A}{s} + \frac{Bs+C}{s^2+4s+5}$$

$$A = \frac{5s+20}{s^2+4s+5} \Big|_{s=0} = 4$$

$$V(s) = \frac{4}{s} + \frac{Bs+C}{s^2+4s+5} = \frac{4s^2+16s+20+Bs^2+Cs}{s^2+4s+5}$$

$$(B+4)s^2 = 0 \quad B = -4$$

$$(C+16)s = 5s \quad C = -11$$

$$V(s) = \frac{4}{s} + \frac{-4s-11}{(s+2)^2+1^2} = \frac{4}{s} + \frac{-4(s+2)}{(s+2)^2+1^2} + \frac{-3(1)}{(s+2)^2+1^2}$$

so $v(t) = \text{unit step response} = (4 - e^{-2t} [4 \cos t + 3 \sin t]) u(t) V$