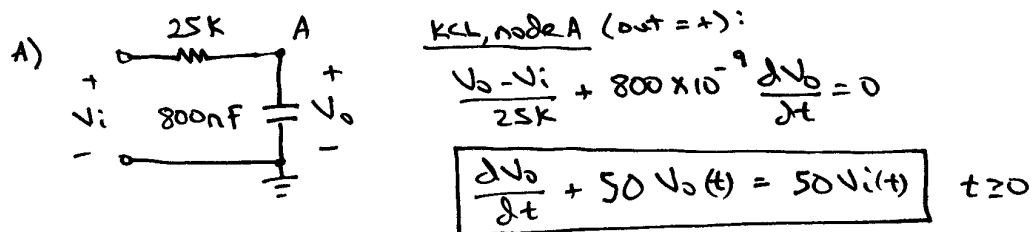


## Solution to Homework Assignment #4

### Problem Assignment:

- 1) For the circuit shown in Problem 13.49a in the Nilsson text:
- Determine the differential equation that represents the system if  $V_i(t)$  is the input voltage and  $V_o(t)$  is the output voltage.
  - Find the unit step response, USR, using the differential equation. Also sketch the USR.
  - Find the impulse response,  $h(t)$ , from the USR using  $h(t) = d/dt(\text{USR})$ . Also sketch  $h(t)$ .
  - Find the transfer function  $H(s) = V_o(s)/V_i(s)$  from the DE in part A
  - Find the unit step response, USR, from  $H(s)$
  - Find the impulse response,  $h(t)$ , from  $H(s)$



B)  $V_i(t) = u(t) = 1$  for  $t \geq 0$ , so  $\frac{dV_o}{dt} + 50 V_o(t) = 50$

Natural response:


$$s + 50 = 0 \text{ (char. eq.) so } V_n = A e^{-50t}$$

Forced response:

$$V_f = B \text{ (constant) so } V_f' = 0 \Rightarrow \text{sub into D.E.: } 0 + 50B = 50$$

$$\text{so } B = V_f = 1$$

(or draw ckt at  $t=0$ )

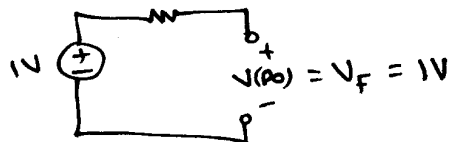

Initial conditions:

$$t=0^- \rightarrow \text{Dead circuit so } V_o(0^-) = 0 = V_o(0^+)$$

Total response:

$$V_o(t) = V_n + V_f = A e^{-50t} + 1$$

$$V_o(0) = 0 = A + 1, \text{ so } A = -1$$

$$\text{USR} = V_o(t) = (1 - e^{-50t}) u(t) \text{ V}$$

$$\begin{aligned}
 c) \quad h(t) &= \frac{d}{dt}[USR] = \frac{d}{dt}[(1 - e^{-50t})u(t)] \\
 &= (1 - e^{-50t})\delta(t) + 50e^{-50t}u(t) \\
 &= (1 - e^0)\delta(t) + 50e^{-50t}u(t)
 \end{aligned}$$

$$h(t) = 50e^{-50t}u(t)$$

$$d) \quad \frac{dV_o}{dt} + 50V_o(t) = 50V_i(t)$$

$$[sV_o(s) - \underbrace{V_o(0)}_0] + 50V_o(s) = 50V_i(s)$$

$$V_o(s) [s + 50] = 50V_i(s)$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{50}{s + 50}$$

$$E) \quad USR = \mathcal{L}^{-1}\left\{\frac{H(s)}{s}\right\} = \mathcal{L}^{-1}\left\{\frac{50}{s(s+50)}\right\} = \mathcal{L}^{-1}\left\{\frac{1}{s} - \frac{1}{s+50}\right\}$$

$$USR = u(t) - e^{-50t}u(t)$$


$$USR = (1 - e^{-50t})u(t)$$

$$F) \quad h(t) = \mathcal{L}^{-1}\{H(s)\} = \mathcal{L}^{-1}\left\{\frac{50}{s+50}\right\}$$

$$h(t) = 50e^{-50t}u(t)$$

2) Repeat problem 1 for the circuit shown in Problem 13.71 in the Nilsson text.

A) Find D.E.

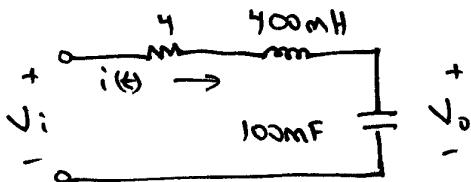

$$\text{KVL: } -V_i + 4i(t) + 0.4 \frac{di}{dt} + V_o = 0$$

$$\text{Capacitor: } i(t) = 0.1 \frac{dV_o}{dt} \text{ so } \frac{di}{dt} = 0.1 \frac{d^2V_o}{dt^2}$$

(sub for  $i(t)$  +  $\frac{di}{dt}$  in KVL)

$$-V_i + 4\left[0.1 \frac{dV_o}{dt}\right] + 0.4\left[0.1 \frac{d^2V_o}{dt^2}\right] + V_o = 0$$

$$\frac{d^2V_o}{dt^2} + 10 \frac{dV_o}{dt} + 25V_o(t) = 25V_i(t) \quad \text{D.E. (tzo)}$$

B) Find the USR:

$$V_i(t) = u(t) = 1 \quad (\text{for } t \geq 0)$$

$$\text{so } \frac{d^2 V_o}{dt^2} + 10 \frac{dV_o}{dt} + 25 V_o(t) = 25$$

natural response:


$$\text{char. eq} \rightarrow s^2 + 10s + 25 = 0$$

$$(s+5)^2 = 0 \rightarrow s_1 = s_2 = -5 \quad (\text{critically damped})$$

$$V_N = (A_1 t + A_2) e^{-5t}$$

forced response:  $V_F = V(\infty)$


$t = \infty$  steady state

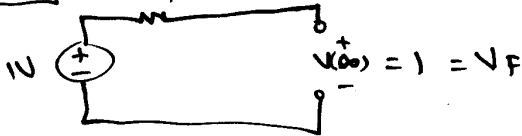

Initial conditions

$$t = 0^- \quad \text{Dead ckt so } V_o(0^-) = 0, \quad i_L(0^-) = 0$$
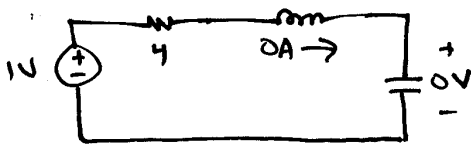
$$t = 0^+ \quad V_o(0^+) = V_o(0^-) = 0, \quad i_L(0^+) = i_L(0^-) = 0$$



$$i(t) = C \frac{dV_o(t)}{dt}$$

so

$$\frac{dV_o(0^+)}{dt} = \frac{i_L(0^+)}{C} = 0$$

total response

$$V_o(t) = V_N + V_F$$

$$V_o(t) = (A_1 t + A_2) e^{-5t} + 1$$

Find  $A_1 + A_2$  using initial conditions ( $V_o(0) = 0, V_o'(0) = 0$ )

$$0 = A_2 + 1 \rightarrow A_2 = -1$$

$\frac{d}{dt}$

$$\frac{dV_o(t)}{dt} = A_1 e^{-5t} + (A_1 t + A_2)(-5e^{-5t}) + 0$$

$$\frac{dV_o(0)}{dt} = 0 = A_1 - 5A_2 = A_1 + 5 \rightarrow A_1 = -5$$

$$\text{so } V_o(t) = [1 - (5t + 1)e^{-5t}] u(t) = \text{USR}$$

c) Find the impulse response:

$$h(t) = \frac{\partial}{\partial t} [uSR] = \frac{\partial}{\partial t} \left[ [1 - (s+1)e^{-st}] u(t) \right]$$

$$h(t) = [1 - (s+1)e^{-st}] \delta(t) [-5e^{-st} + 5(s+1)e^{-st}] u(t)$$

$$h(t) = [1 - (0+1)e^0] \delta(t) + 25te^{-st} u(t)$$

$$h(t) = 25te^{-st} u(t) = \text{impulse response}$$

d) Find  $H(s)$  from D.E.

$$\frac{\partial^2 V_o}{\partial t^2} + 10 \frac{\partial V_o}{\partial t} + 25V_o(t) = 25V_i(t)$$

$$\mathcal{L} \left\{ \left[ s^2 V_o(s) - \underbrace{sV_o(0)}_0 - \underbrace{V_o'(0)}_0 \right] + 10 \left[ sV_o(s) - \underbrace{V_o(0)}_0 \right] + 25V_o(s) \right\} = 25V_i(s)$$

$$V_o(s) [s^2 + 10s + 25] = 25V_i(s)$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{25}{(s+5)^2}$$

e) Find uSR from  $H(s)$ :

$$uSR = \mathcal{L}^{-1} \left\{ \frac{H(s)}{s} \right\}$$

$$\frac{H(s)}{s} = \frac{25}{s(s+5)^2} = \frac{A}{s} + \frac{B}{(s+5)^2} + \frac{C}{s+5} = \frac{1}{s} - \frac{5}{(s+5)^2} - \frac{1}{s+5}$$

$$\text{so } uSR = u(t) - 5te^{-st} u(t) - e^{-st} u(t)$$

$$uSR = [1 - (st+1)e^{-st}] u(t)$$

f) Find  $h(t)$  from  $H(s)$

$$h(t) = \mathcal{L}^{-1} \{ H(s) \} = \mathcal{L}^{-1} \left\{ \frac{25}{(s+5)^2} \right\} = 25te^{-st} u(t) = \text{impulse response}$$

For problems 3, 4, 5, and 6 below use a graphical approach in evaluating the convolution integral. Include sketches to illustrate each part of the solution as well as the related calculations. Sketch the final result as well.

- 3) Problem 2.4-18, parts a,c,f, and g in the Lathi text (Hint: Invert  $x_1$  rather than  $x_2$  on part g.)  
 Find and sketch  $c(t) = x_1(t) * x_2(t)$  for the waveforms below.



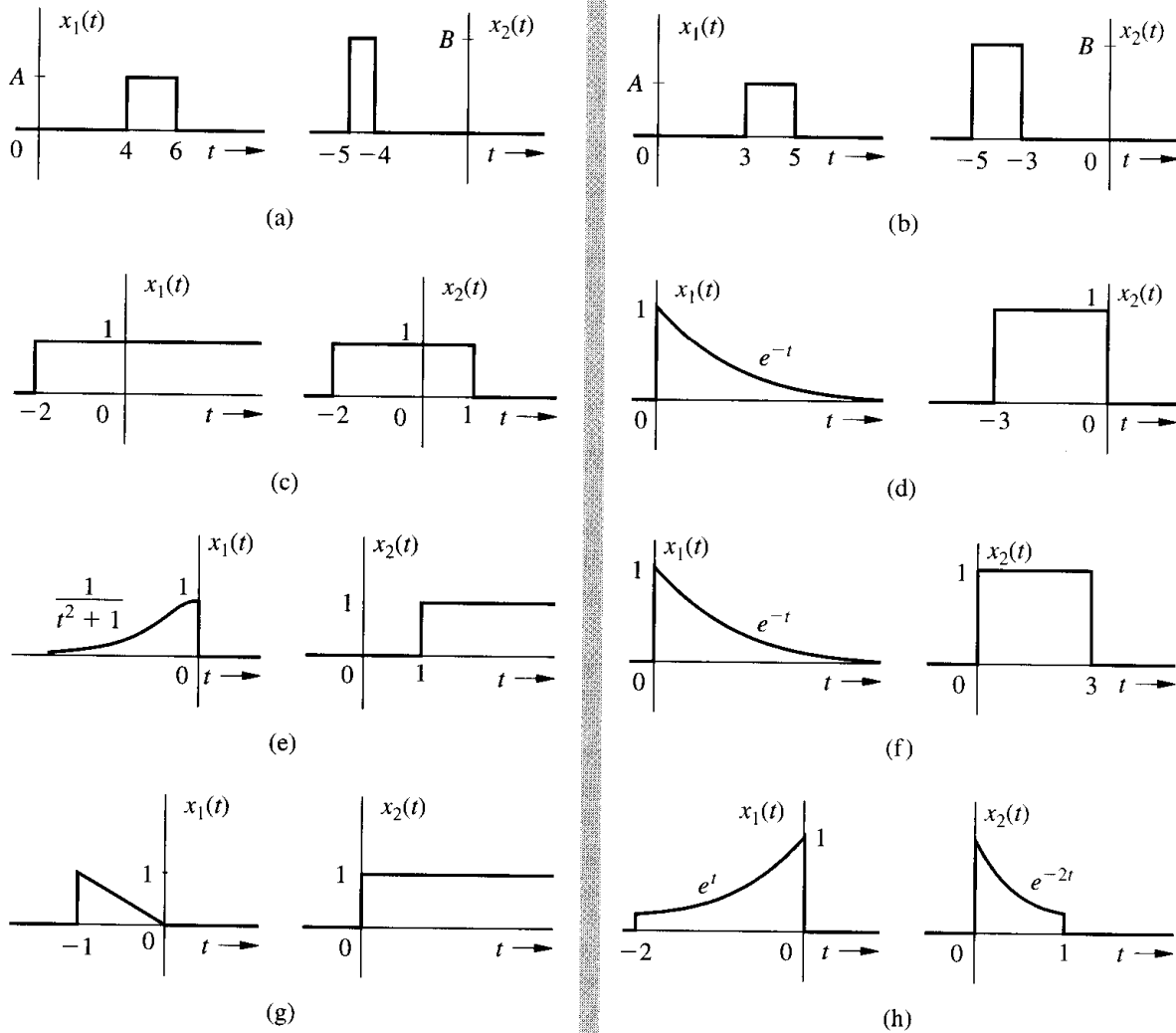
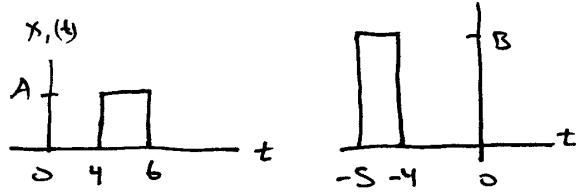


Figure P2.4-18

2.4-18a) Find  $x_1(t) * x_2(t) = c(t)$

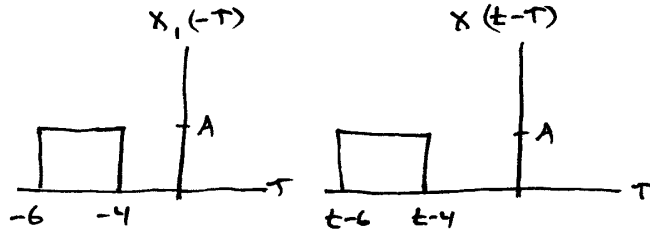


Solution:

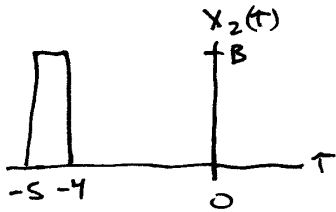

A)  $t < -1 \rightarrow$  no overlap

so  $c(t) = 0$  ( $t < -1$ )


B)  $-1 \leq t \leq 0$

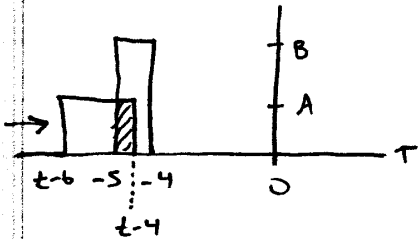

$$c(t) = \int_{-5}^{t-4} AB \delta\tau = AB\tau \Big|_{-5}^{t-4} = AB(t-4) - AB(-5)$$

$c(t) = AB(t+1)$  ( $-1 \leq t \leq 0$ )


C)  $0 \leq t \leq 1$

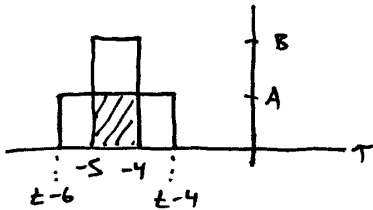

$$c(t) = \int_{-5}^{-4} AB \delta\tau = AB\tau \Big|_{-5}^{-4} = AB(-4) - AB(-5)$$

$c(t) = AB$  ( $0 \leq t \leq 1$ )

D)  $1 \leq t \leq 2$

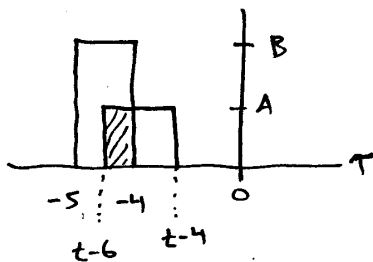


$$c(t) = \int_{t-6}^{-4} AB \delta\tau = AB\tau \Big|_{t-6}^{-4} = AB(-4) - AB(t-6)$$

$c(t) = AB(2-t)$  ( $1 \leq t \leq 2$ )

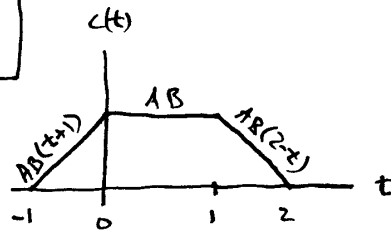E)  $t \geq 2 \rightarrow$  no overlap so  $c(t) = 0$

Summary:

$$c(t) = \begin{cases} 0 & t < -1 \\ AB(t+1) & -1 \leq t \leq 0 \\ AB & 0 \leq t \leq 1 \\ AB(2-t) & 1 \leq t \leq 2 \\ 0 & t \geq 2 \end{cases}$$



(b)

$$\begin{aligned}
 c(t) &= \int_{1.5+t}^{2.5} AB \, d\tau = AB(1-t) & 0 \leq t \leq 1 \\
 c(t) &= \int_{1.5}^{2.5+t} AB \, d\tau = AB(t+1) & -1 \leq t \leq 0 \\
 c(t) &= 0 & \text{for } |t| \geq 1
 \end{aligned}$$

(c)

$$\begin{aligned}
 c(t) &= \int_{-1+t}^{2+t} d\tau = 3 & t > -1 \\
 c(t) &= \int_{-2}^{2+t} d\tau = t+4 & -1 \geq t \geq -4 \\
 c(t) &= 0 & t \leq -4
 \end{aligned}$$

(d)

$$\begin{aligned}
 c(t) &= \int_t^{3+t} e^{-\tau} \, d\tau = e^{-t}(1 - e^{-3}) = 0.95e^{-t} & t \geq 0 \\
 &= \int_0^{3+t} e^{-\tau} \, d\tau = 1 - e^{-(3+t)} = 1 - 0.0498e^{-t} & 0 \geq t \geq -3 \\
 &= 0 & t \leq -3
 \end{aligned}$$

(e)

$$\begin{aligned}
 c(t) &= \int_{-\infty}^{-1+t} \frac{1}{\tau^2+1} \, d\tau = \tan^{-1}(t-1) + \frac{\pi}{2} & t \leq 1 \\
 c(t) &= \int_{-\infty}^0 \frac{1}{\tau^2+1} \, d\tau = \tan^{-1} \tau \Big|_{-\infty}^0 = \frac{\pi}{2} & t \geq 1
 \end{aligned}$$

(f)

$$\begin{aligned}
 c(t) &= \int_0^t e^{-\tau} \, d\tau = 1 - e^{-t} & 0 \leq t \leq 3 \\
 c(t) &= \int_{t-3}^t e^{-\tau} \, d\tau = e^{-(t-3)} - e^{-t} & t \geq 3 \\
 c(t) &= 0 & t \leq 0
 \end{aligned}$$

(g) This problem is more conveniently solved by inverting  $x_1(t)$  rather than  $x_2(t)$ 

$$\begin{aligned}
 c(t) &= \int_t^{t+1} (\tau - t) \, d\tau = \frac{1}{2} & t \geq 0 \\
 c(t) &= \int_0^{t+1} (\tau - t) \, d\tau = \frac{1}{2}(1 - t^2) & 0 \geq t \geq -1 \\
 c(t) &= 0 & \text{for } t \leq -1
 \end{aligned}$$

(h)  $x_1(t) = e^t$ ,  $x_2(t) = e^{-2t}$ ,  $x_1(\tau) = e^\tau$ ,  $x_2(t-\tau) = e^{-2(t-\tau)}$ .

$$\begin{aligned}
 c(t) &= \int_{-1+t}^0 e^\tau e^{-2(t-\tau)} \, d\tau = e^{-2t} \int_{-1+t}^0 e^{3\tau} \, d\tau = \frac{1}{3}[e^{-2t} - e^{t-3}] & 0 \leq t \leq 1 \\
 c(t) &= \int_{-1+t}^t e^\tau e^{-2(t-\tau)} \, d\tau = e^{-2t} \int_{-1+t}^t e^{3\tau} \, d\tau = \frac{1}{3}[e^t - e^{t-3}] & 0 \geq t \geq -1 \\
 c(t) &= \int_{-2}^t e^\tau e^{-2(t-\tau)} \, d\tau = e^{-2t} \int_{-2}^t e^{3\tau} \, d\tau = \frac{1}{3}[e^t - e^{-2(t+3)}] & -1 \geq t \geq -2 \\
 c(t) &= 0 & t \leq -2
 \end{aligned}$$


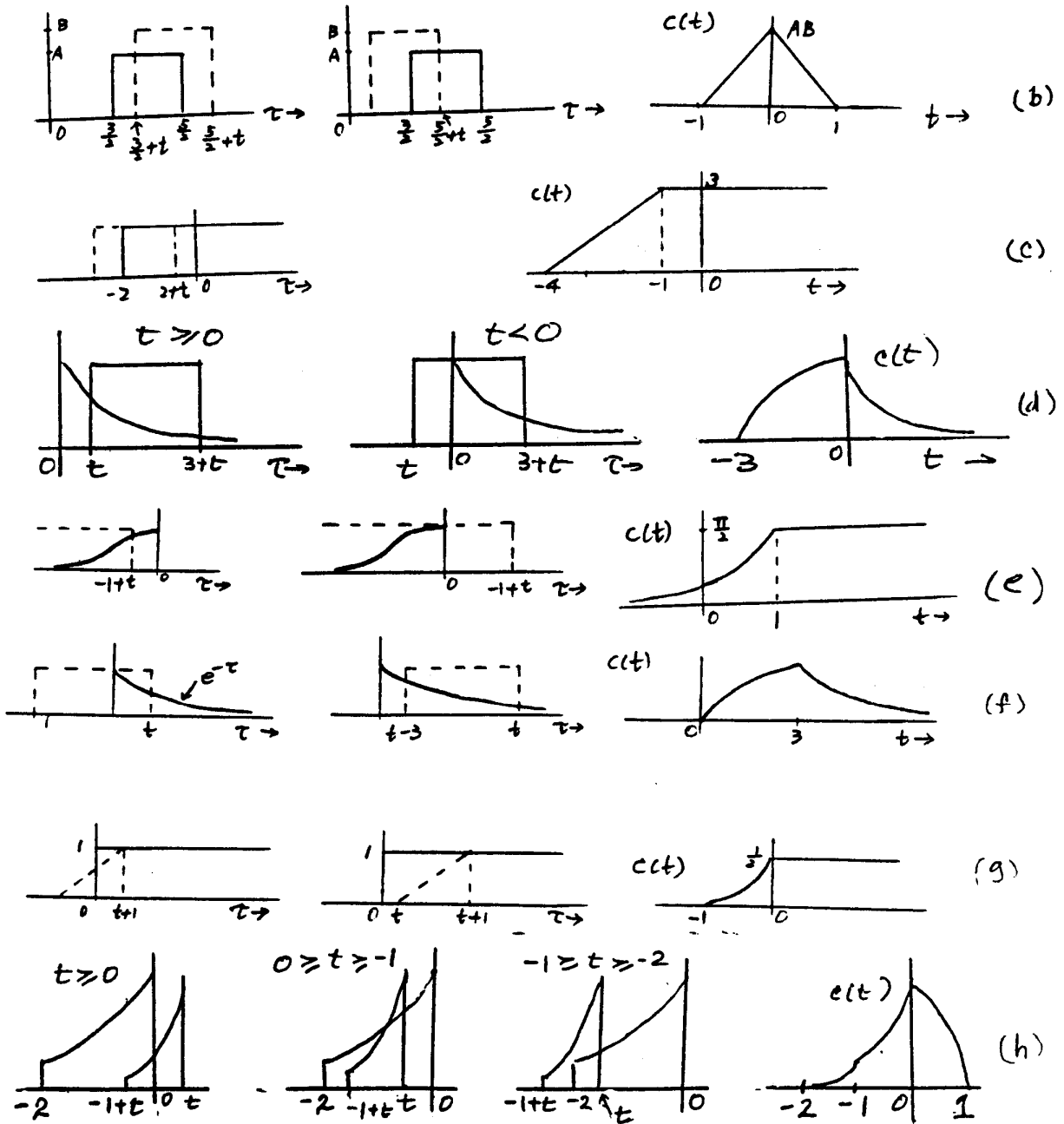


Fig S2.418

4) Problem 13.59b in the Nilsson text

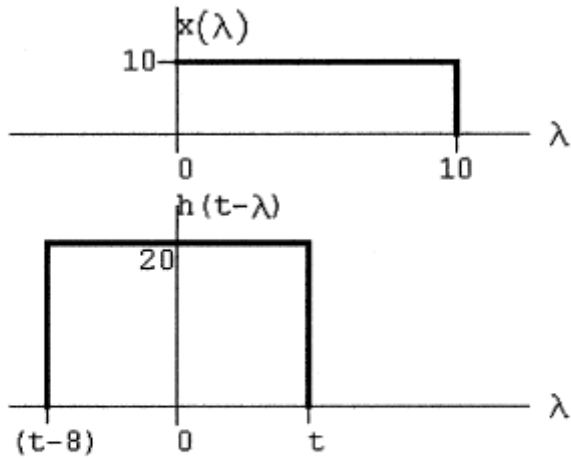


$$y(t) = 0 \quad t < 0$$

$$0 \leq t \leq 8: \quad y(t) = \int_0^t 200 \, d\lambda = 200t$$

$$8 \leq t \leq 10: \quad y(t) = \int_{t-8}^t 200 \, d\lambda = 200(t - t + 8) = 1600$$

$$10 \leq t \leq 18: \quad y(t) = \int_{t-8}^{10} 200 \, d\lambda = 200(18 - t)$$

$$18 \leq t < \infty: \quad y(t) = 0$$

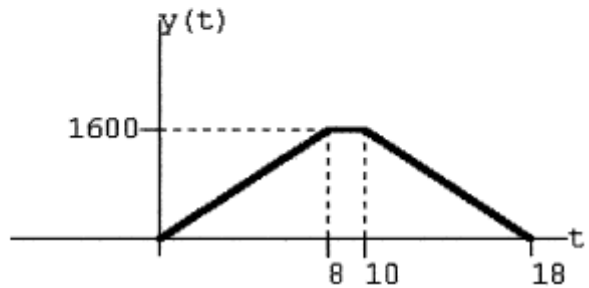

5) Problem 13.61 in the Nilsson text

P 13.61 [a]  $-1 \leq t \leq 4$ :

$$v_o = 20 \int_0^{t+1} 3\lambda d\lambda = 30\lambda^2 \Big|_0^{t+1} = 30t^2 + 60t + 30$$

 $4 \leq t \leq 7$ :

$$\begin{aligned} v_o &= 20 \int_0^5 3\lambda d\lambda + 20 \int_5^{t+1} (20 - \lambda) d\lambda \\ &= 30\lambda^2 \Big|_0^5 + 400\lambda \Big|_5^{t+1} - 10\lambda^2 \Big|_5^{t+1} \\ &= -10t^2 + 380t - 610 \end{aligned}$$

 $7 \leq t \leq 12$ :

$$\begin{aligned} v_o &= 20 \int_{t-7}^5 3\lambda d\lambda + 20 \int_5^{t+1} (20 - \lambda) d\lambda \\ &= 30\lambda^2 \Big|_{t-7}^5 + 400\lambda \Big|_5^{t+1} - 10\lambda^2 \Big|_5^{t+1} \\ &= -40t^2 + 800t - 2080 \end{aligned}$$


 $12 \leq t \leq 19$ :

$$\begin{aligned} v_o &= 20 \int_{t-7}^{t+1} (20 - \lambda) d\lambda = 400\lambda \Big|_{t-7}^{t+1} - 10\lambda^2 \Big|_{t-7}^{t+1} \\ &= -160t + 3680 \end{aligned}$$

 $19 \leq t \leq 27$ :

$$\begin{aligned} v_o &= 20 \int_{t-7}^{20} (20 - \lambda) d\lambda = 400\lambda \Big|_{t-7}^{20} - 10\lambda^2 \Big|_{t-7}^{20} \\ &= 10t^2 - 540t + 7290 \end{aligned}$$


[b]

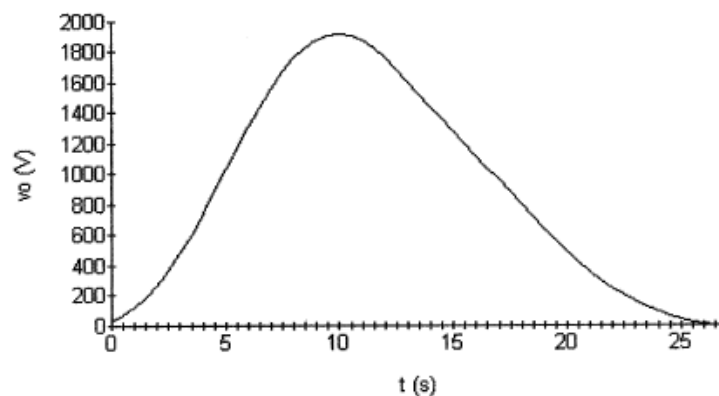

6) Problem 13.57 in the Nilsson text

P 13.57  $H(s) = \frac{V_o}{V_i} = \frac{1}{s+1}$ ;  $h(t) = e^{-t}$

For  $0 \leq t \leq 1$ :

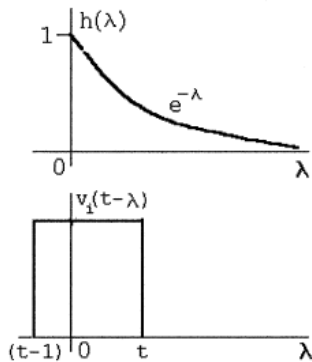

$$v_o = \int_0^t e^{-\lambda} d\lambda = (1 - e^{-t})V$$

For  $1 \leq t \leq \infty$ :

$$v_o = \int_{t-1}^t e^{-\lambda} d\lambda = (e - 1)e^{-t}V$$

7) Repeat problem 13.57 using Laplace transforms. Specifically, find  $H(s) = V_o(s)/V_i(s)$  and then find  $v_o(t) = \mathcal{L}^{-1}\{H(s)V_i(s)\}$ .

$V_i = [u(t) - u(t-1)]'$  so  $V_i(s) = \frac{1}{s} - \frac{e^{-s}}{s} = \frac{1-e^{-s}}{s}$

S-Domain circuit:  $V_i(s) \rightarrow \frac{1}{s} \rightarrow V_o(s) = V_i(s) \left[ \frac{1}{s+1} \right]$  so  $H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{s+1}$

(Note:  $h(t) = \mathcal{L}^{-1}\left\{\frac{1}{s+1}\right\} = e^{-t}u(t)$ )

$V_o(s) = H(s) \cdot V_i(s)$   
 $V_o(s) = \left(\frac{1}{s+1}\right) \left[\frac{1}{s} - \frac{e^{-s}}{s}\right] = \frac{1}{s(s+1)} - \frac{e^{-s}}{s(s+1)}$

$V_1(s) = \frac{1}{s(s+1)} = \frac{1}{s} + \frac{-1}{s+1}$

so  $V_1(t) = u(t) - e^{-t}u(t) = (1 - e^{-t})u(t)$

$V_2(s)$  is a delayed (+ negated) version of  $V_1(s)$ , so  
 $V_2(s) = -(1 - e^{-(t-1)})u(t-1)$

$V_o(s) = V_1(s) + V_2(s)$   
 so  $V_o(t) = (1 - e^{-t})u(t) - (1 - e^{-(t-1)})u(t-1)$

or  $V_o(t) = \begin{cases} 0 & t < 0 \\ 1 - e^{-t} & 0 \leq t < 1 \\ (1 - e^{-t}) - (1 - e^{-(t-1)}) = -e^{-t} + e^{-(t-1)} & t \geq 1 \end{cases}$