

PSPICE Assignment #2

PSPICE Analysis of Sequential Logic Circuits

Reference:

Schematic Capture Using Cadence PSPICE by Herniter.

Handout: Sample PSPICE Report

PSPICE Example: “*Modified Sequence Counter*” (File: MOD_SEQ.OPJ)

Assignment Description:

Use ORCAD Capture version 9.0 or later for this assignment.


1. Custom Modified Sequence Counter:

- A. Design (by hand) a modified sequence counter using JK flip-flops to count out the last five unique digits of your EmplID in the order in which they occur and then repeats. For example, if your EmplID is 8345952, then your counting sequence is 3, 4, 5, 9, 2 and repeat. If you do not have five unique digits in your EmplID, use all of your unique digits (in the order in which they occur) followed by other digits of your choice for a total of five digits. Neatly show all steps in your design.
- B. Use PSPICE to simulate the circuit above. Use a 10 kHz clock to run the counter and use another clock to initialize the counter to the 3rd count in your sequence. Generate a timing diagram using PROBE that shows 10 cycles of the 10 kHz clock as well as the initialization signal and the outputs. Also add a bus within PROBE which gives the decimal value of the count.
- C. Zoom in on a small portion of the first cycle in the timing diagram above and print a new timing diagram that clearly illustrates the effect of the initialization signal.
- D. Change the frequency of the 10 kHz clock in part B to 25 MHz and again generate a timing diagram that shows 10 cycles of the clock as well as the initialization line, output signals, and the bus specifying the count. Is the count correct at all times? Discuss the results in your report.
- E. Repeat step 1B with the 10 kHz clock replaced by a clock generator using a 555 timer with a frequency equal to the last 4 non-zero digits of your SSN in Hz (any duty cycle is OK). Using your values of R_A , R_B , and C , show the calculations for T_L , T_H , T , D , and f in your report (or on the schematic). Adjust the time for the transient response so that 10 cycles of the count are again displayed. Use two cursors to measure the period T of the clock and add labels to the graph displaying the measured values of T and f .


(continued)

2. Frequency Division Using 7490 Decade Counters:

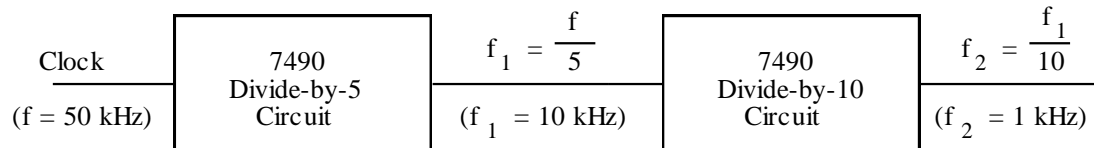- A. Use PSPICE to connect two 7490 decade counters as shown below. The first counter should be configured as a divide-by-five circuit and the second counter as a divide-by-ten circuit with a symmetric output. Use a clock input with a frequency of 50 kHz. Hint: To properly initialize the counter, apply a LO input to R91 and R92 and apply an initialization pulse to R01 and R02. The initialization signal should go HIGH for at least twice the length of the propagation delay of the 7490 (or $2 \times 25 \text{ ns} = 50 \text{ ns}$) as shown below.



Initialization signal:

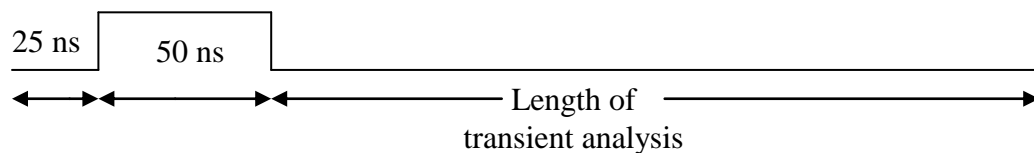

- B. Generate a timing diagram within PROBE showing the waveforms f , f_1 , and f_2 . Show 50 cycles of f (this should correspond to 10 cycles of f_1 , and 1 cycle of f_2).

Extra Credit:

D flip-flop design and simulation: (worth up to 25 extra points on this assignment)

Repeat Problem 1 (parts A and B only) using D flip-flops (7474) designed using the state equation method. Show all of your design work.